
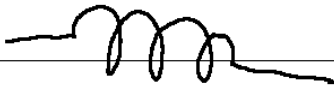


First Day - Syllabus Review

 R

 C

 L

} Parts of a
circuit

- Buy textbook
- Office hours: 11 AM - Noon / 1 - 2 P.M (every weekday)

MUST PASS FINAL WITH A C!

CZ - EEAE I

CII - EEFE II

Electronic Devices - EEFE III

- 4 Regular test, then final (so 5 total tests)
- Schedule on back of syllabus.


Submitting Homework

- One .pdf file (can include all pages)

Ch. 1 Basic Concepts


1.3 Charge and Current

- Electric current, I or $i(t)$ $\frac{dQ}{dt}$ $\frac{dQ/dt}{dQ/dt}$
- Amount of moving electric charges, Q or $q(t)$ per time [Ampere = coulomb/sec]
- $I = Q/t$ or $i(t) = d(q)/dt$
- $Q = I \cdot t$ or $q = \int_{t_1}^{t_2} i(t) dt$

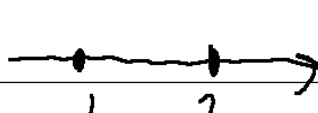Direction polarity  $I_{12} = -I_{21}$

1.4 Polarity

- Voltage, V or $V(t)$
- Amount of energy, W or $w(t)$, per charge required to move charges across two locations
- [Volt = Joule/Coulomb]

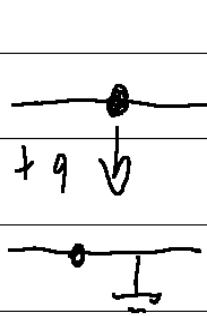Direction of polarity  $V_1(t)$ $V_2(t) = 0$ Kinetic energy

$$V = W/Q \text{ or } V(t) = dw(t)/dq$$

$$W = V \cdot Q \text{ or } W = \int_{q(t_1)}^{q(t_2)} V(t) dq$$

$$W = \underbrace{V}_{\text{height}} \cdot \underbrace{Q}_{\text{mass}}$$

↓ kinetic energy

$$V_{12} = V_1 - V_2 = -V_{21}$$


potential = 1 Volt

1.5 Power


- Electrical power P or $P(t)$
- Amount of energy per time absorbed (consumed) by a circuit element [$\text{Watt} = \text{Joule/second}$]
- $P(t) = \frac{dw(t)}{dt} = \frac{dw(t)}{dq} \frac{dq}{dt} = v(t) i(t)$
 $w = \int_{t_1}^{t_2} p(t) dt = \int_{t_1}^{t_2} v(t) i(t) dt$

Sign convention

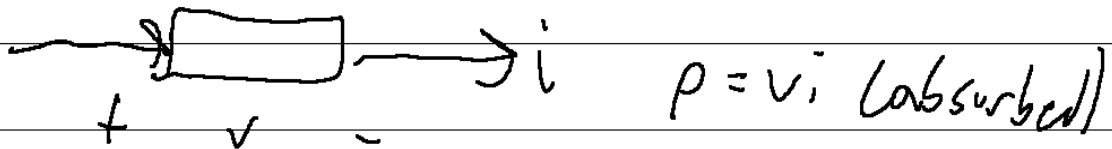- Absorption (consumption): passive sign convention



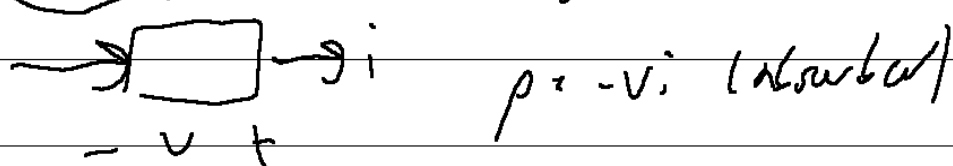
- Supply (generation): active sign convention



$$\text{J/s} = \text{W}$$

- Power balance

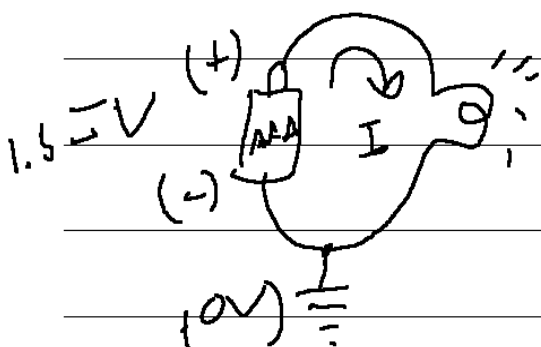
$$\sum P(t)_{\text{supplied}} = \sum P(t)_{\text{absorbed (in a network)}}$$



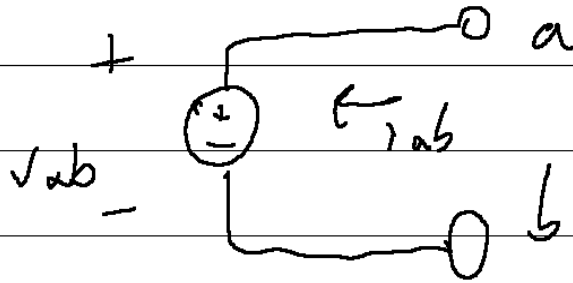
1.6 Circuit Elements (sources)

Independent sources

- (Ideal) independent voltage source: v_{ab} is independent of i_{ab}



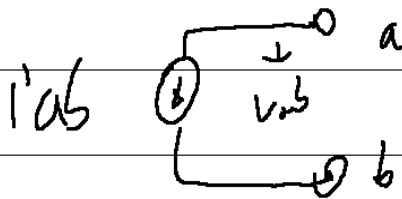- (Ideal) independent current source: i_{ab} is independent of v_{ab}



Dependent sources


- Output voltage (or current) dependent on input voltage



Dependent Sources

Output voltage (or current) dependent on
input voltage (or current):
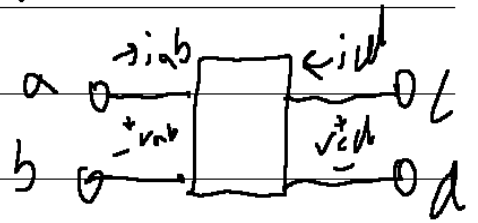
$$v_{cd} \text{ (or } i_{cd}) = f(v_{ab} \text{ or } i_{ab})$$



Gain



Voltage-controlled voltage source: voltage gain $[V/V]$

—//— Current source: transconductance $[A/V]$

Current-controlled voltage source: transresistance $[V/A]$

—//— Current source: current gain $[A/A]$

Symbol

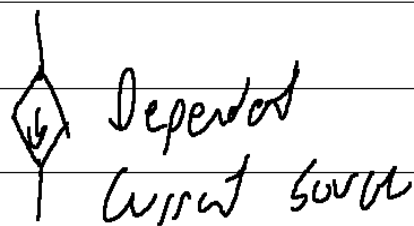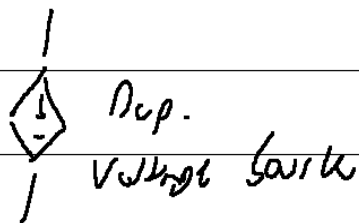



Ch.2 Basic Laws

2.2 Ohm's Law

• Resistor: a device to dissipate electrical energy into other forms of energy

• Resistance / Conductance


• Ohm's Law: $v_{ab} = R \cdot i_{ab}$

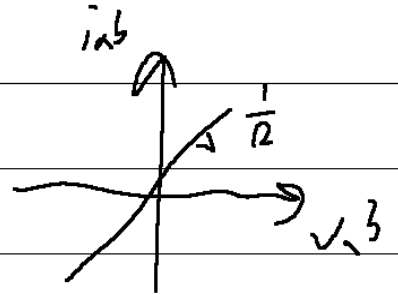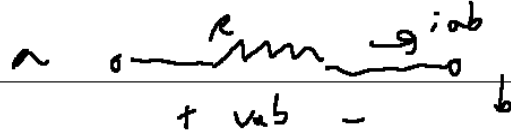

(\neq passive sign convention)

• Resistance, R [ohm (Ω) = volt/Ampere]

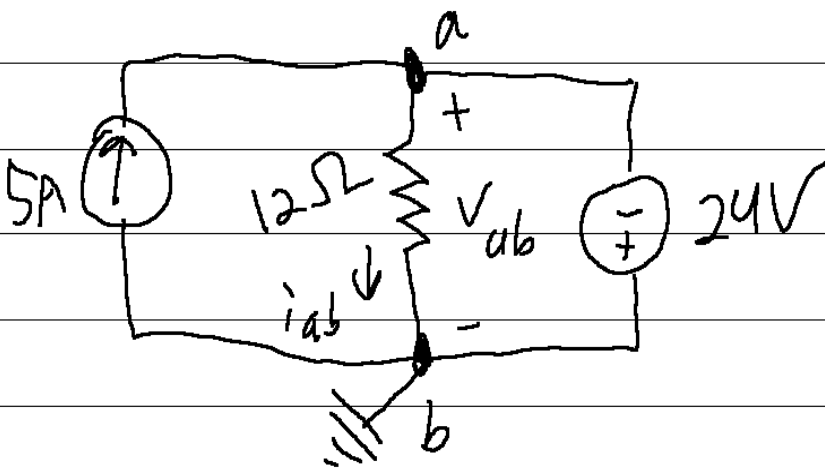
(conductance, G ($= 1/R$) [Siemens (S) or mho (Ω^{-1})])



① $V_{ab} = -24V$

② $V_{ab} = R \cdot i_{ab} \rightarrow i_{ab} = V_{ab}/R = -24/12 = -2A$

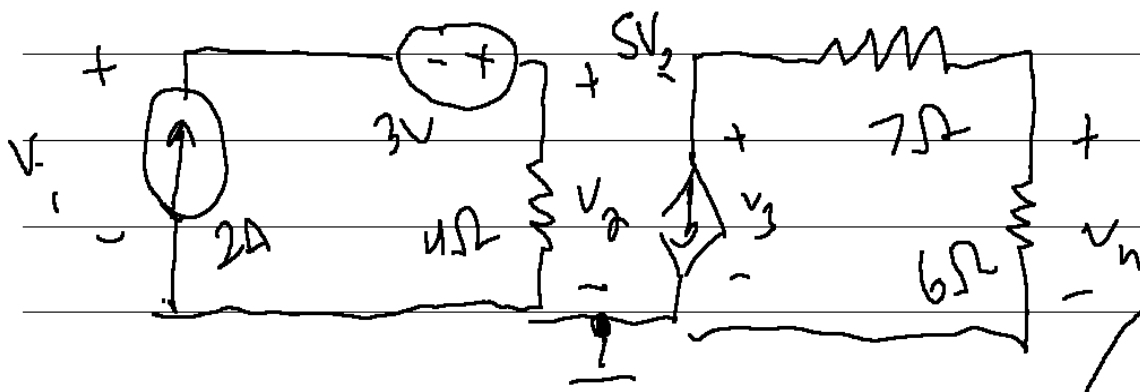③ $P_{12\Omega} = i_{ab} \cdot V_{ab} = -2 \times -24 = 48W$ (absorbed)



Ohm's Law: $V = iR$

① (KVL) $-V_1 - 3 + V_2 = 0 \rightarrow V_1 = 5 \text{ (V)}$

② $V_2 = 2 \times 4 = 8 \text{ (V)}$


③ (KVL) $-V_3 + V_4 + (-5V_2 \times 7) = 0 \rightarrow V_3 = - \text{ (V)}$

④ $V_4 = 5 \times V_2 = (5 \times 8) \times 6 = -240 \text{ (V)}$

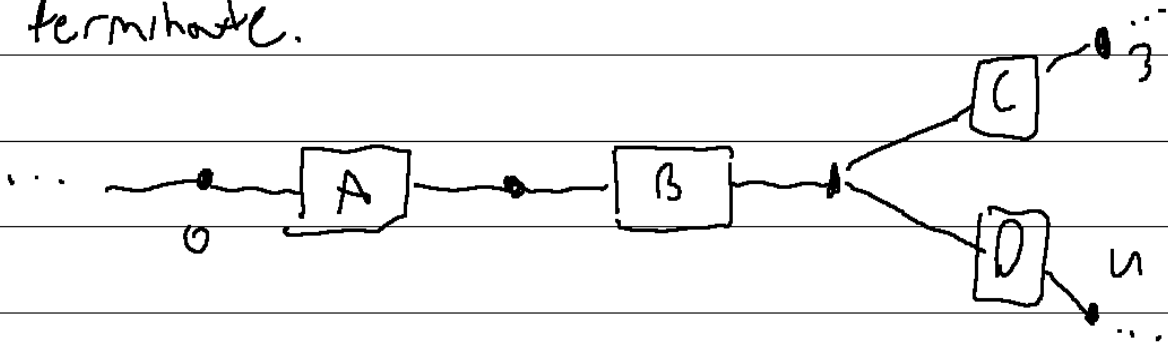2.3 Nodes, Branches, Loops


Nodes

- ① Branch: a circuit element and attached line segment
- ② Node: termination of one or more branches
- ③ Junction: a node where 3 or more branches terminate.



Loops

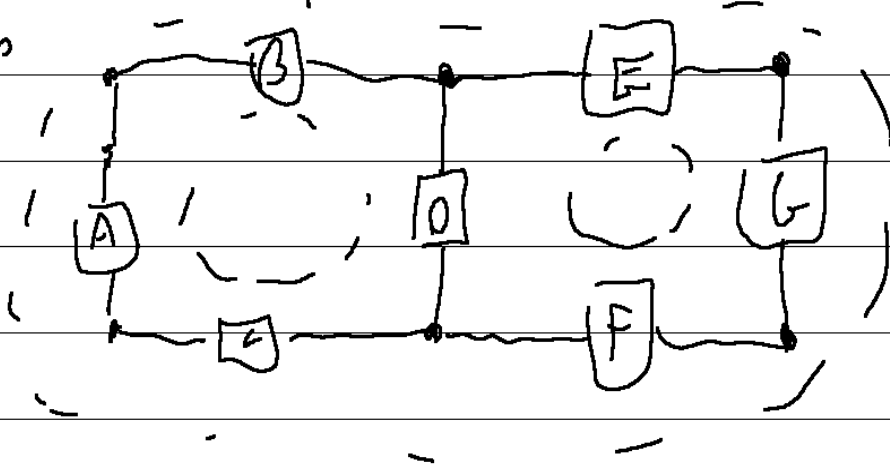
- ① Loop: a closed path of branches
- ② mesh: a loop that does not enclose another loop



Short/Open

- ① Short circuit: multiple nodes are connected (resistance between nodes are zero)
- ② open circuit: multiple nodes are isolated

(resistance) between nodes are ∞)

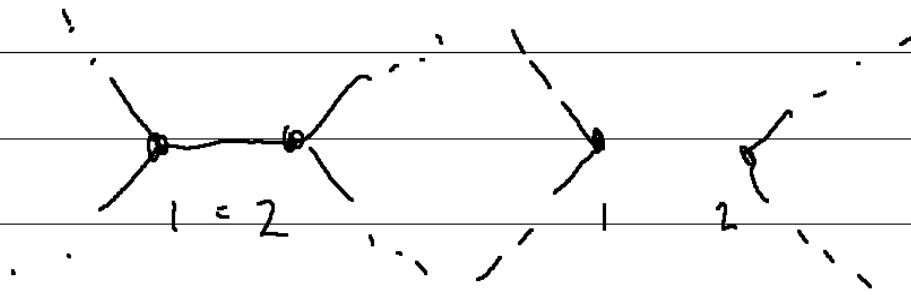


2.1 Kirchhoff's Law

Kirchoff's Current Law (KCL)

① sum of entering currents and sum of leaving currents over a closed surface is same

② $i_1 + i_2 + i_3 = i_4$

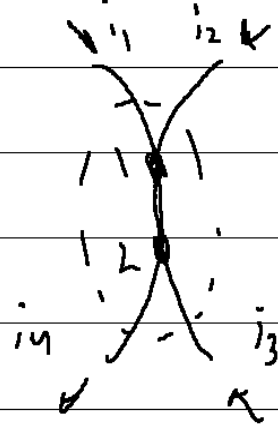
$$\Rightarrow \begin{pmatrix} i_1 + i_2 + i_3 - i_4 = 0 \\ -i_1 - i_2 - i_3 + i_4 = 0 \end{pmatrix}$$



Kirchoff's Voltage Law (KVL)


sum of all voltage drops along a closed loop is zero.
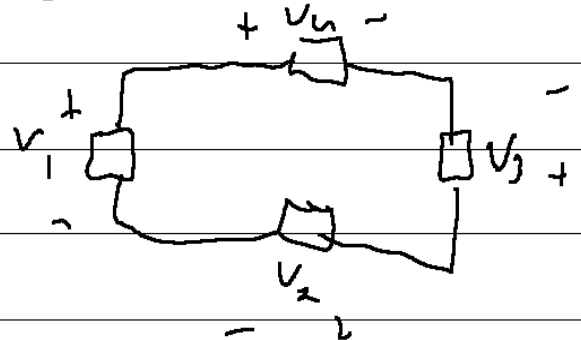
$$\begin{pmatrix} V_1 - V_2 + V_3 - V_4 = 0 \\ -V_1 + V_2 - V_3 + V_4 = 0 \end{pmatrix}$$



Attendance Worksheet (continuing from Wednesday)

② 1KVL

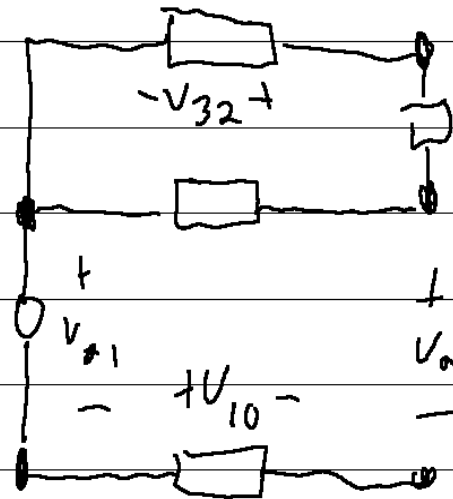

$$V_{10} = -2V \quad (V_1 - V_0 = -2)$$

$$V_{20} = 1$$

$$V_{30} = 18$$

$$V_{40} = 6 \quad (V_4 - V_0 = 6)$$

$$V_a = ?$$

① $V_a (= V_{40}) = 6(V)$

② (1KVL) $-V_{10} - V_{21} - V_{32} - \sqrt{43} + V_a = 0$

$$V_{21} = V_2 - V_1 = V_{20} - \sqrt{10} = 1 - (-2) = 3(V)$$


$$V_{32} = V_{30} - V_{20} = 17$$

$$V_{43} = \sqrt{40} - \sqrt{30} = -12$$

$$\rightarrow V_a = 6(V)$$

Attn wu (Friday)

(Sources, Ohm, KVL/KCL)

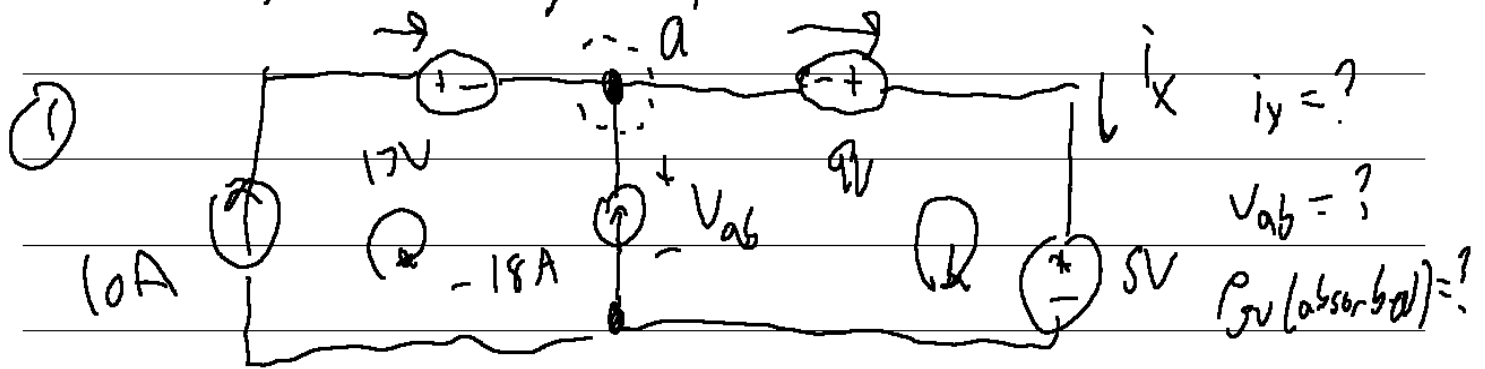


① $-10 - (-18) + i_x = 0 \rightarrow i_x = -8(A)$ (KCL)

② $-V_{ab} - 4 + 5 = 0 \rightarrow V_{ab} = -4(V)$ (KVL)

③ $P_{5V} = 5 \cdot i_x = -40(W)$ (absorbed) (pass)

(2)

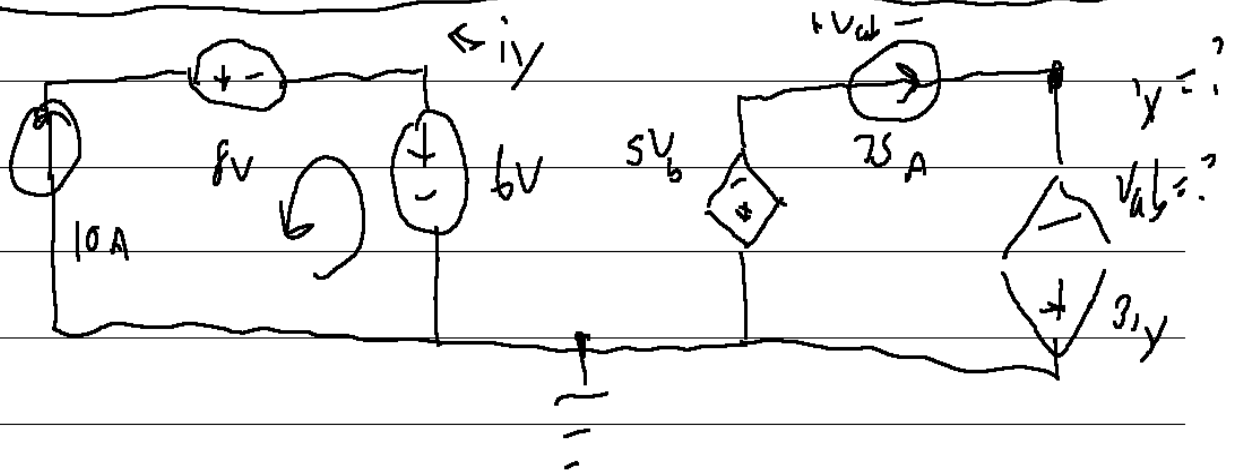


① $-10 - i_y = 0 \rightarrow i_y = -10(A)$ (KCL)

② $V_{ab} - 3i_y + 5V_x = 0 \rightarrow V_{ab} =$
 $-V_y + 8 + 6 = 0 \rightarrow V_y = 14$ (KVL)

2.5 Series resistors and Voltage Division

(1) "Single-loop" (series circuit)

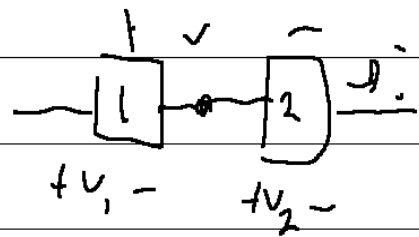

① Series connection:

Same current through each component

Different voltage drop across each element

② $V = V_1 + V_2 = IR_1 + IR_2 = IR_s$ ($R_s = R_1 + R_2$; equiv resistance)

(2) Series elements

① Resistance: $R_s = R_1 + R_2 + \dots + R_N$

② Conductance: $G_s = \frac{1}{\frac{1}{G_1} + \frac{1}{G_2} + \dots + \frac{1}{G_N}}$

③ Inductance: $L_s = L_1 + L_2 + \dots + L_N$

④ Capacitance: $C_s = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$

⑤ Voltage Division $\rightarrow V_s \frac{R_2}{R_1 + R_2}$

Voltage is divided proportionally to each resistance

$$V_K = \left(\frac{R_K}{R_1 + R_2 + \dots + R_K + \dots + R_N} \right) V = \frac{R_K}{R_s} V$$


2.6 Parallel Resistors and Current Division

(1) "two-node" parallel (16)

① Parallel connection:

Same voltage across each element, V

Different current through each element

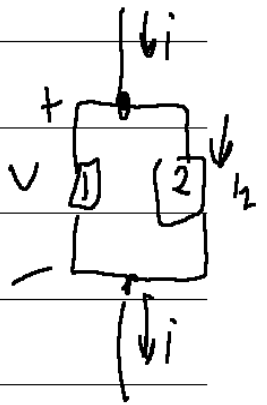

$$\textcircled{2} i = i_1 + i_2 = \frac{V}{R_1} + \frac{V}{R_2} = \frac{V}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \text{ (equiv resistance)}$$

(2) Parallel elements

$$\textcircled{1} \text{ Resistance: } R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$


$$\textcircled{2} \text{ Conductance: } G_p = G_1 + G_2 + \dots + G_N$$

$$\textcircled{3} \text{ Inductance: } L_p = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$

$$\textcircled{4} \text{ Capacitance: } C_p = C_1 + C_2 + \dots + C_N$$

 (3) Current Division

③ Current V divided inversely-proportionally to each resistance.



Test #1 Practice Samples

(1) $i_1 = 96/10 = 9.6 \text{ A}$ [Ohm's Law]

(2) $-90 + 25 \cdot i_2 + 30 + 15 \cdot i_2 = 0$

$i_2 = 1.5 \text{ A}$

(3) $V_{ab} = 25 \cdot i_2 + 30$

$\rightarrow V_{ab} = 67.5 \text{ (V)}$

①

(1) $V_{ab} = V_{oc} = 60 \text{ (V)}$

(2) $i_b = 60/60 = 1 \text{ (A)}$

(3) $-i_a + i_b + i_c = 0$

$(i_c = 4 \cdot i_b)$

$\rightarrow i_a = 5 \text{ (A)}$

(4) $i_c = 4 \cdot i_b = 4 \text{ (A)}$

(5) $P_{60V} = -60 \cdot i_a = -300 \text{ [W]}$ absorbed
(active)

②

(1) $-24 + 16i_1 + 4V_1 = 0$

(2) $V_1 = -0.5i_1 + 4$

$\rightarrow V_1 = -6 \text{ (V)}$

$i_1 = 3 \text{ A}$

③

(1) [Take KVL over the whole loop]

(4)

$$\textcircled{1} -100 + 2i_1 + 8i_1 + 5i_1 + 9i_1 - 20 = 0$$

$$\Rightarrow i_1 = 5(A)$$

$$\textcircled{2} -V_{ab} + 10 \times 0 - 30 + 5i_1 - 20 + 9i_1 = 0$$

$$\rightarrow V_{ab} = 20(V)$$

$$\textcircled{1} V_{ab} = 6 \cdot 10 = 60(V)$$

(5)

$$\textcircled{2} V_{bc} = 4 \cdot V_{ab} = 240(V)$$

$$\textcircled{3} V_{ac} = V_{ab} + V_{bc} = 300(V)$$

$$\textcircled{4} V_{ec} = V_{bc} = 240(V)$$

$$\textcircled{5} P_{6A} = -6 \times 300 = 1,800(W) \text{ absorbed}$$

(or 1.8 kW)

$$\textcircled{1} i: -12 + 5i + 10i + 5i + 20i + 2 - 15 = 0$$

(9)

$$i = 0.5(A)$$

$$\textcircled{2} V_1 = 5i = 2.5(V)$$

$$V_2 = 20i = 10(V)$$

$$\text{(or } V_2 = \left(\frac{20}{5+10+5+20} \right) 20 = 10)$$

$$\textcircled{1} -12 - 5i_a - 10i_a - 15i_a - 20i_a + 2 - 15 = 0$$

$$\rightarrow i_a = -0.5(A)$$

$$① 54 + 18 = 72$$

$$36 // 72 = 24$$

$$(16 + 24 = 40)$$

$$V_2 = \left(\frac{24}{16 + 24} \right) 60 = 48(V)$$

$$② V_1 = \left(\frac{18}{54 + 18} \right) V_2 = 12(V)$$

option 4 =

$$\begin{cases} -80 + 16i_1 + 36i_2 = 0 & (V_2 = 36i_2) \\ -36i_2 + 54i_3 + 16i_3 & (V_1 = 18i_3) \end{cases}$$

$$\begin{cases} -60 + 16i_1 + 54i_2 + 16i_3 = 0 \end{cases}$$

$$① i_x = \left(\frac{1/6}{1/6 + 1/18} \right) 12 = 8(A)$$

$$② -V_x = 3i_x = +24V$$

$$③ -V + 12 \cdot 4 - V_x + 6i_x - 5V_x = 0$$

$$\rightarrow V = 240(V)$$

$$④ P_{12A} = (12 \cdot 240) = -2,880(W) \text{ absorbed (active)}$$

$$① V = 36(V)$$

$$② 6 // 3 = 2, R_{ab} = 4 + 2 = 6$$

$$i_y = 36 / 6 = 6(A)$$

$$③ i_x = \left(\frac{1/4}{1/4 + 1/2} \right) i_y = 2(A)$$

$$④ -i + i_y - 2i_x = 0$$

$$\rightarrow i = 2(A)$$

Ch. 3 method of analysis

3.2 Nodal analysis


(1) Node Voltage (NV)

- ① Ref node: ref for all other nodes (node $\neq 0$: $v_0 = 0$)
- ② Node Voltage: $V_{ko} = V_k - V_0 = V_k$ (Voltage of node k)
- ③ Node Voltage eqs: a set of eqs with NVs as variables

$$(V_1, V_2, \dots, V_K)$$

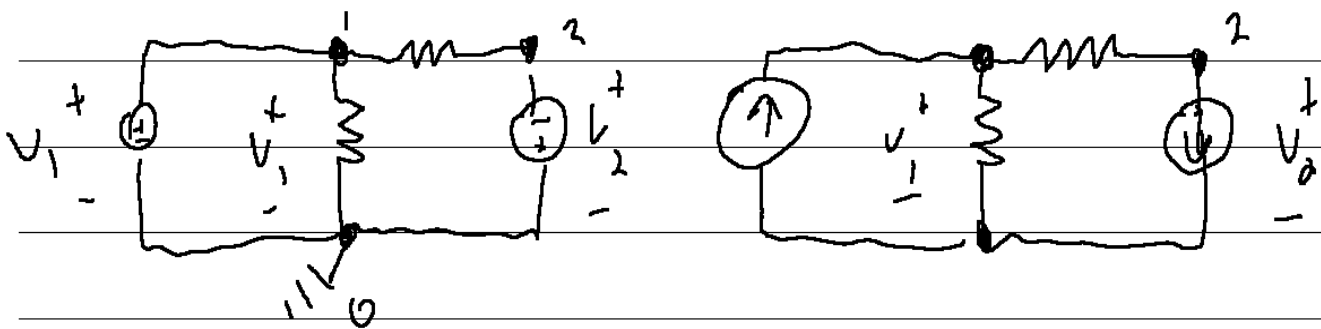(2) NV eqs

- ① one KVL eq: for each node connected to ref node by a path of voltage sources
- ② one KCL eq: for each node NOT connected to voltage source



Test #1 Solutions

- ①
- a) 0.02 (A)
 - b) -8 V
 - c) $-0.04 \text{ W (absorbed)}$
 - d) -16 W (absorbed)

- ②
- a) 25 A
 - b) 250 V?
 - c) 150 V
 - d) 240 V

- ③
- a) 2 A
 - b) 24 V
 - c) 20 V
 - d) -24 W absorbed

- ④
- a) 3 A
 - b) -30 V
 - c) -7 V
 - d) -2 A

3.3 Node analysis with Voltage Sources

1) Supernode

- ① A group of nodes connected to each other by voltage source(s), but NOT directly to ref node by voltage source(s).
- ② One KCL eq: for a surface enclosing a supernode
- ③ KVL eq(1): for other node(s) within supernode in terms of "principal node".

(2) Network analysis by NV

(1) procedure

- ① Identify ref node and Supernode(s).
- ② # of NV eqs = # of total nodes - 1.
- ③ Build a set of NV eqs.

HW Notes

#1) No need for V_x

#2) Supernode 2, 3

* Just complete matrix





3.4 Mesh currents

(1) Mesh current (MC)

- ① Mesh current: i_x at the outer path of x th mesh (i_j, i_k)
- ② Branch current: current at a shared branch (i_j, i_k)
- ③ MC eqs: a set of eqs with MCs as variables (i_1, i_2, \dots, i_k)

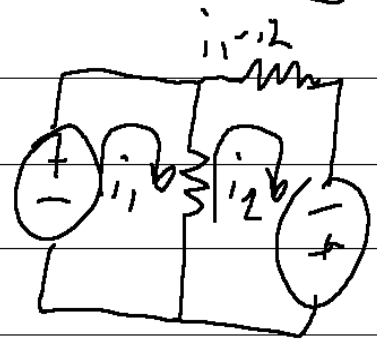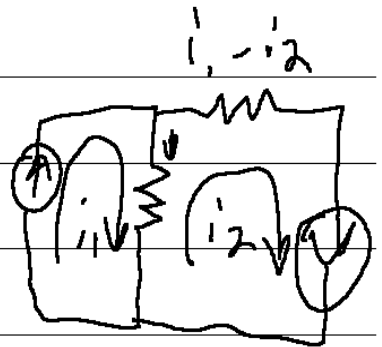(2) MC eqs

- ① One KCL eq: for each branches with current source(s)
- ② One KVL eq: for each loop without current source(s)





3.5 Mesh analysis with Current Sources

(1) Supermesh

- ① A group of meshes showing a current source with other meshes: none of which contains current source(s) i.e. outer loop
- ② One KVL eq: for each mesh
- ③ KCL eq(s): for branches within supermesh in terms of "principal mesh".

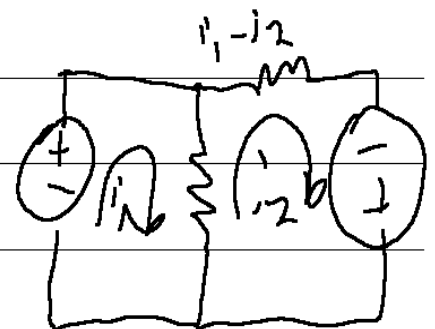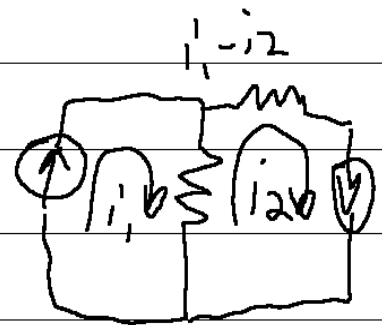(2) Network analysis procedure by MC

- ① Identify each mesh and supermesh(es)
- ② # of MC eqs = # of mesh.
- ③ Build MC eqs.




Ch. 4 Circuit Theorems


4.2 Linearity

(1) Linear network


① Linearity:

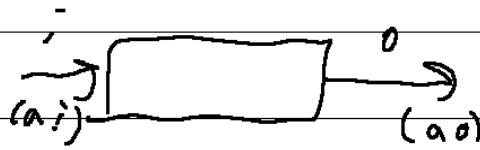

② Superposition:

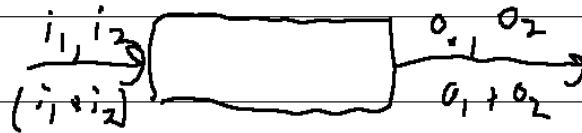

③ Time invariance:

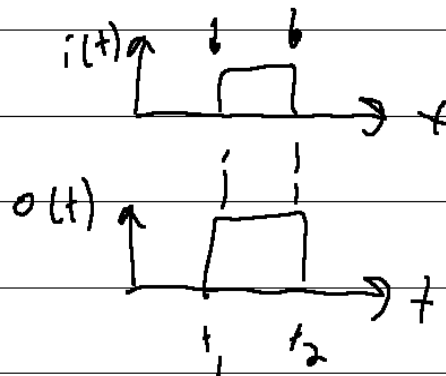

4.3 Superposition

① Indep. Voltage Source \rightarrow short -ckt ($V=0$)

Indep. current \rightarrow open -ckt ($I=0$)

Dep. source \rightarrow no change

② Response to each indep. source at a time

\rightarrow total response = sum of each response

4.4 Source Transformation


(1) Sources

① Practical Voltage Source:


An ideal voltage source with a series resistance

② Practical current source:

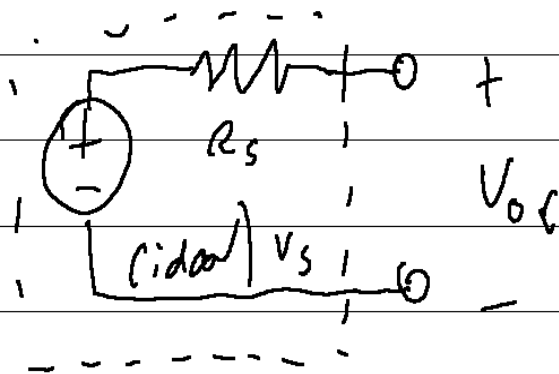An ideal current source with a parallel resistance




Practical

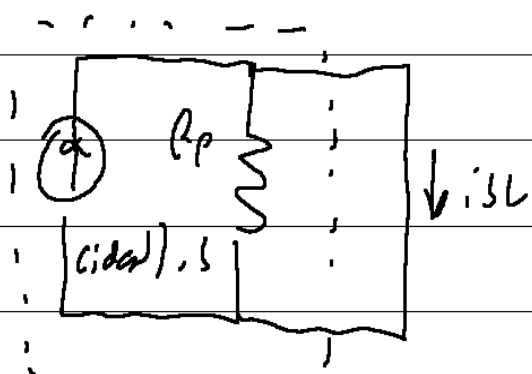

Practical


(V_{oc} : open-circuit voltage, I_{sc} : short-circuit current)

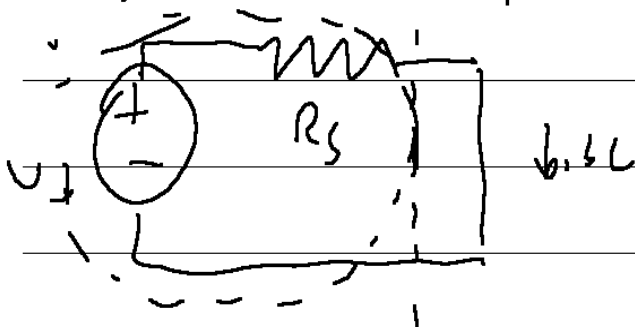(2) ideal vs. practical (with extreme loads)



(load resistance = 0)
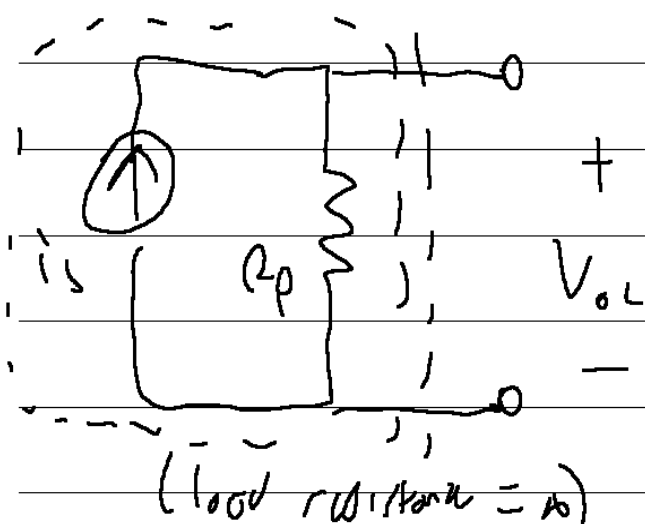
$$V_s = I_{sc} \times R_s$$
$$\left(\begin{array}{l} f_{finite} = f_{finite} \times f_{finite}(\text{practical}) \\ f_{finite} = \infty \times 0 \text{ (ideal)} \end{array} \right)$$




$$i_s = V_{oc} / R_p$$

$$f_{finite} = f_{finite} / f_{finite} \text{ (parallel)}$$

$$f_{finite} = \infty / \infty \text{ (ideal)}$$

(3) Source Transformation

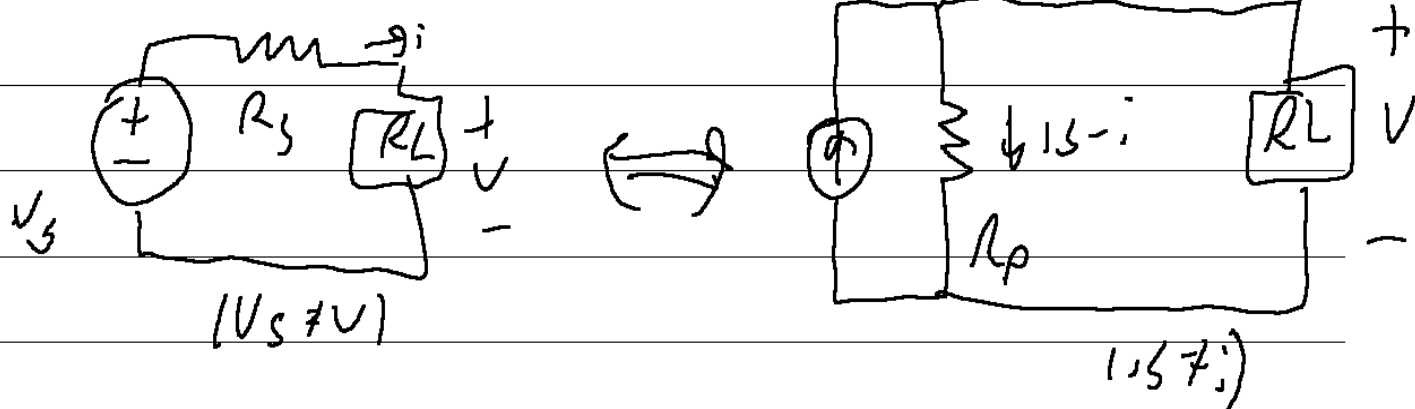


① Voltage source: $V = V_s - R_s i$

Current source: $V = R_p (i_s - i) = R_p i_s - R_p i$

$\rightarrow V_s = i_s R$ (if $R_s = R_p = R$)


② Conversion:

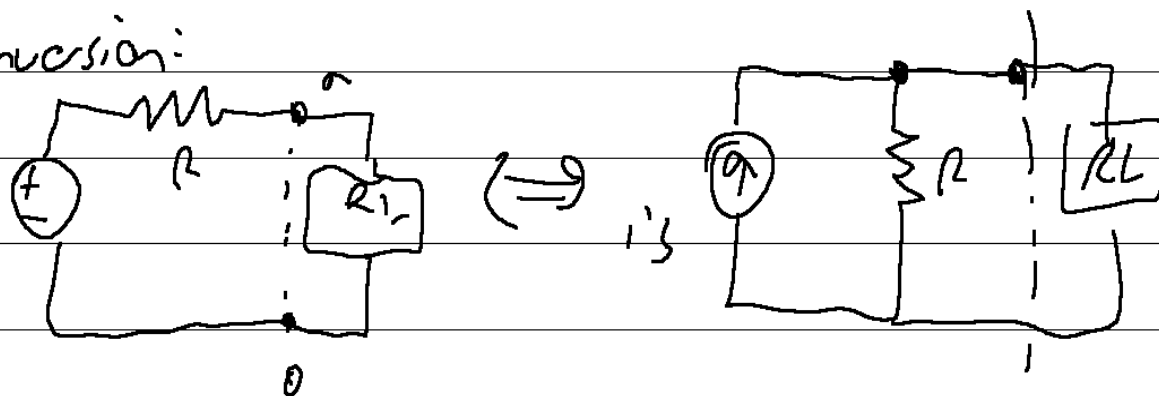


(4) Effect of R_S , R_P on ideal sources

① Ideal voltage source with R_P :


equiv to ideal voltage source itself

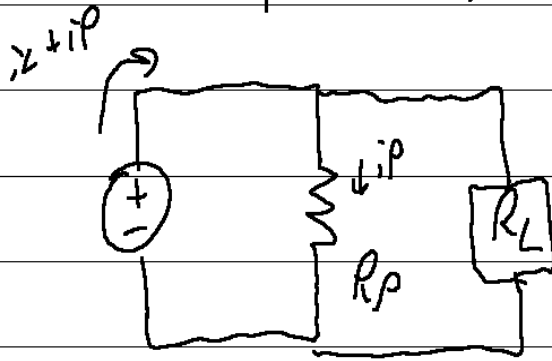

$$V_S = i_L R_L \\ = i_P R_P$$

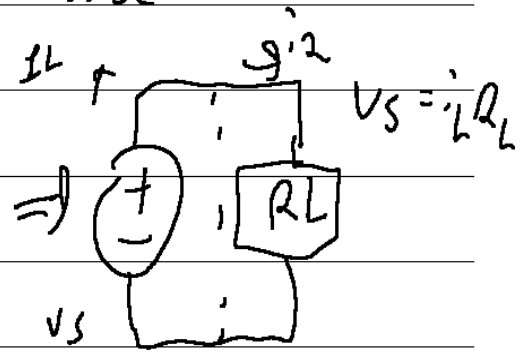

4.5 Thevenin Theorem

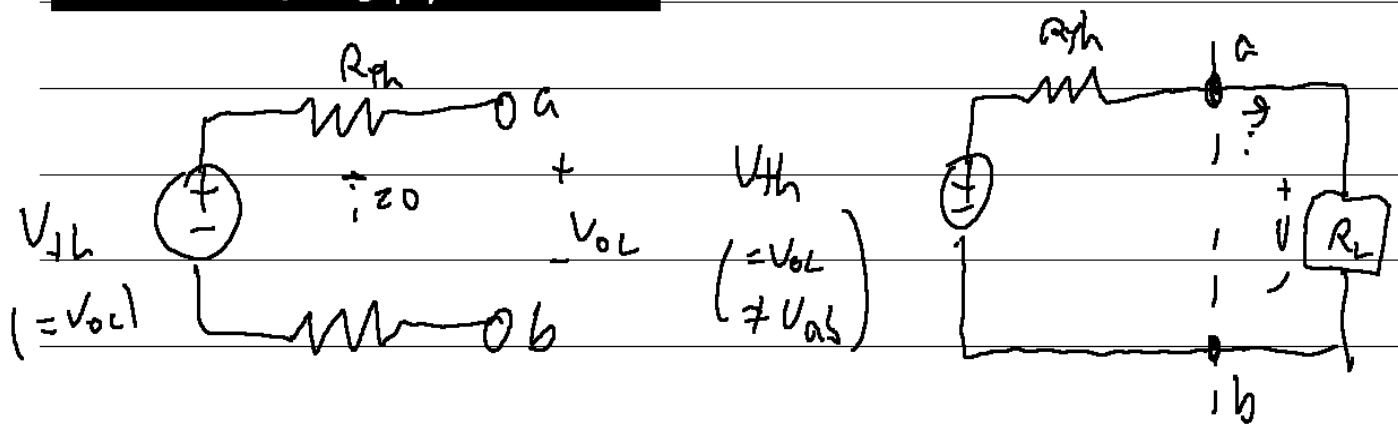

(1) Components

① Thevenin voltage source, V_{th} :

open-ckt ($i=0$), equiv voltage source

② Thevenin resistor, R_{th} :

equiv. resistor with all indep. sources are deactivated; can be found by replacing load with an imaginary source.

(2) Thevenin equiv. ckt


① Equiv. practical voltage source seen from open terminals

② terminal characteristic (with R_L): $V_{th} = V + R_{th}i$

③ V_{th} ($= V_{oc}$) and R_{th} are indep. from R_L :

once R_L is attached, not open-ckt anymore
($i \neq 0$, $V_{th} \neq V$)

4.6 Norton Theorem

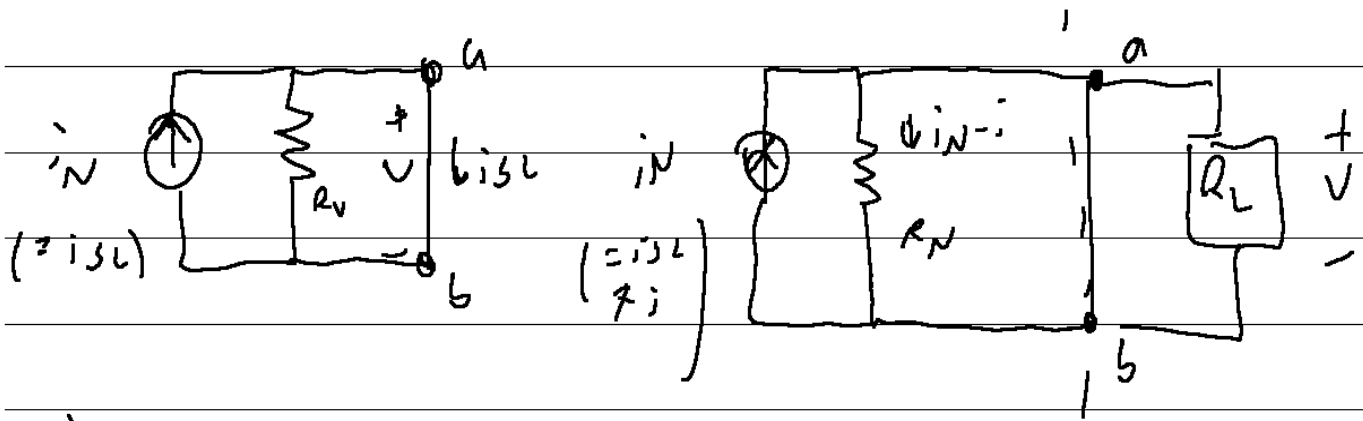

(1) Components

① Norton current source, i_N :

closed-circuit ($v=0$), equiv current source

② Norton resistor, R_N :

equiv. resistor with all indep. sources deactivated;
can be found by replacing load with a imaginary
source.


(3) Source transformation (when $R_{Th} = R_N = R$)

$$V_{Th} = i_N \cdot R \quad (V_{oc} = i_{sc} \cdot R)$$

4.6 Max Power Transfer

(1) Theorem: $P_L = R_L i^2 = R_L \left(\frac{V_S}{R_S + R_L} \right)^2$



$$(P = V_i i = i^2 R = \frac{V^2}{R})$$

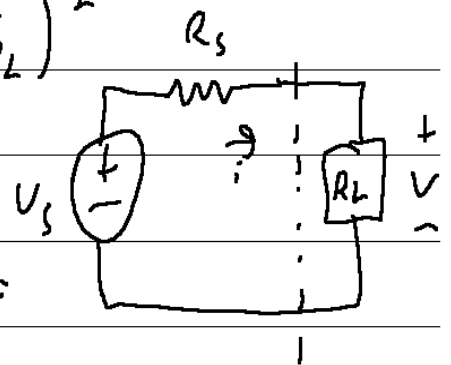

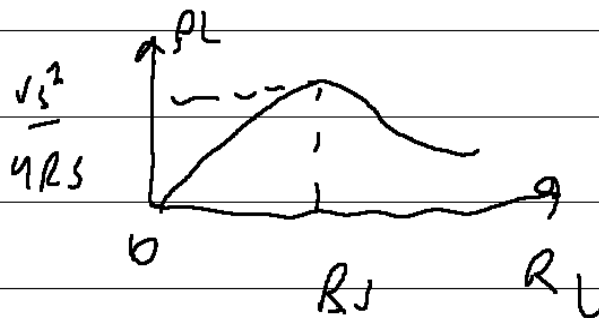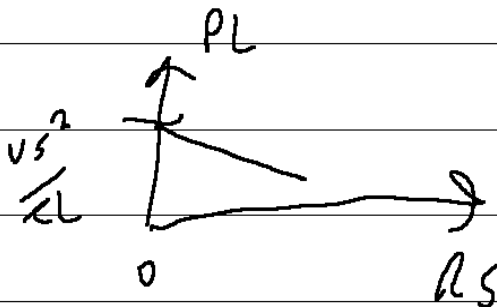(2) Max power delivery to load R_L :

$$R_S = 0: P_L = \frac{V_S^2}{R_L} \quad (\text{for ideal source})$$

$$R_L = R_S: P_L = \frac{V_S^2}{4R_S} \quad (\text{for practical source})$$




Test #2 Sample Problems

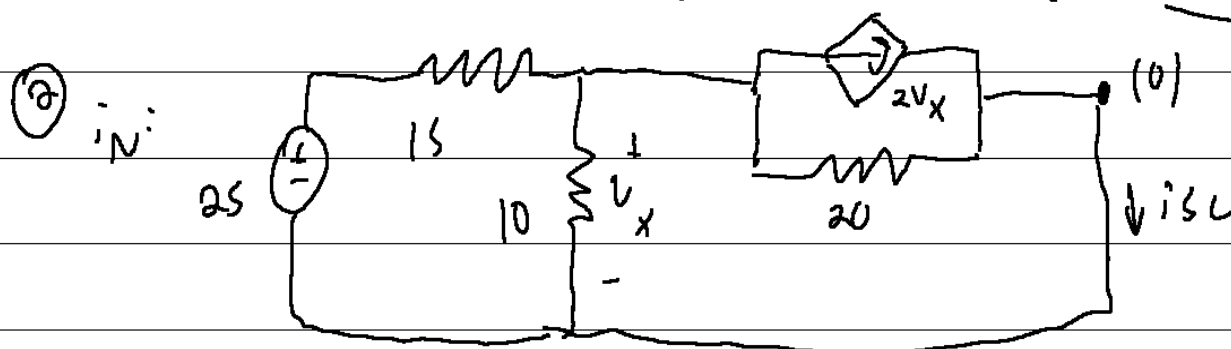9) ① V_{th} : KCL

$$\frac{(V_x - 25)}{15} + \frac{V_x}{10} + 0 = 0 \rightarrow V_x = 10$$

$$(KCL) -2V_x + (V_{oc} - V_x)/20 = 0 \rightarrow V_{oc} = 410(V)$$




$$(KCL) \frac{(V_x - 25)}{15} + \frac{V_x}{10} + i_N = 0$$

$$(KVL) V_x = (i_N - 2V_x) 20$$

ohm's Law

$$\rightarrow i_N = \frac{410}{266} (A)$$

③ $R_N (=R_{th})$:

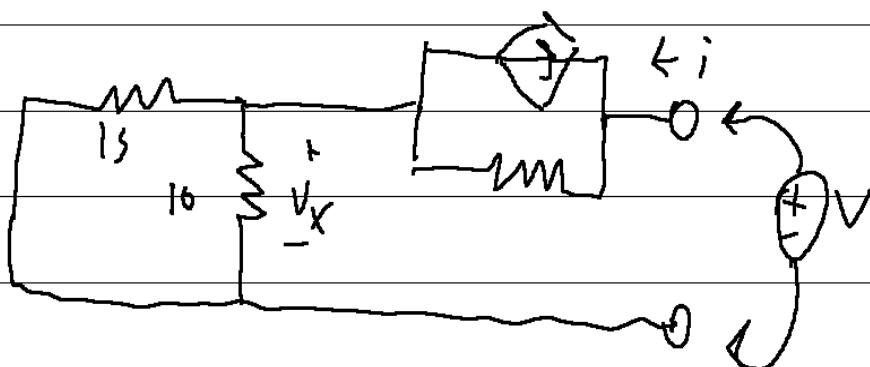

$$(KVL) -V_x + V - 20(2V_x - i) = 0$$

$$V_x = (6/15)i$$


$$\rightarrow R_N (=R_{th}) = V/i = 26 \Omega$$

$$\textcircled{4} P_L = \frac{V_{th}^2}{4R_{th}} \quad (\text{when } R_L = R_{th})$$

$$= \frac{(410)^2}{4 \times 266} \text{ [W]}$$


$$10) \text{ } \circ V_{th}: -1 \text{ k} 2 \text{ k} \cdot i_B + 0.004 V_L = 0$$
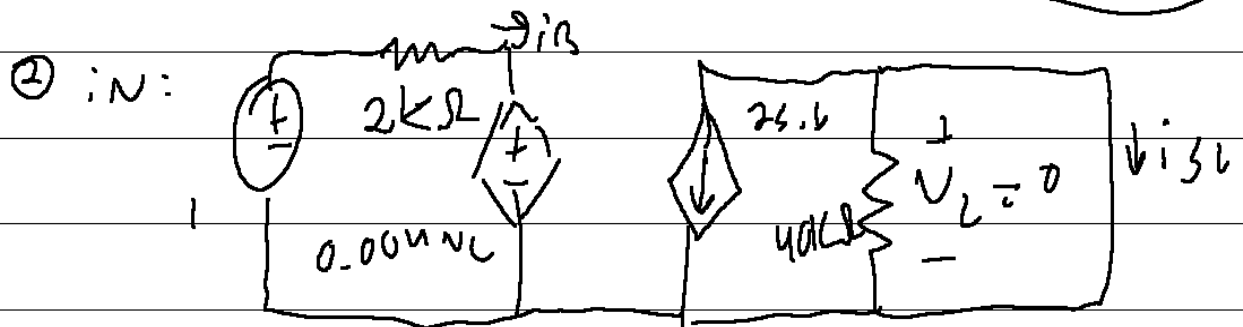
$$V_L = -25 i_B \times 40 \text{ k} = -625 = \underline{\underline{V_{OL}}}$$




$$i_B = \frac{1}{2 \text{ k}} = 0.5 \text{ mA}, \quad i_{sc} = -25 i_B = -12.5 \text{ mA}$$

③ $R_N (= R_{th})$:


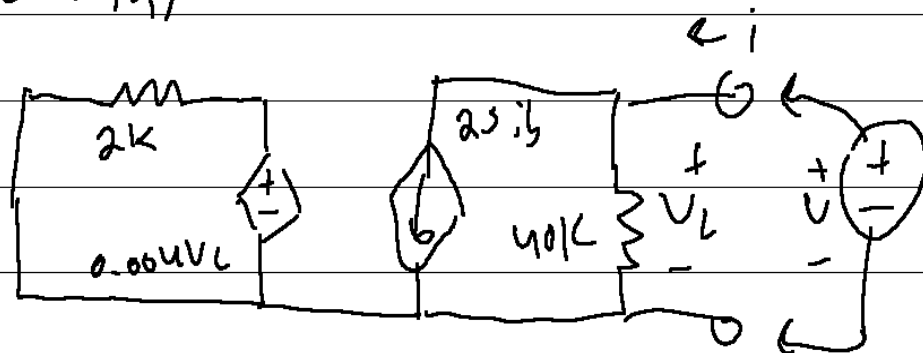


$$\left. \begin{aligned} 25.6 + \frac{V}{40 \text{ k}} - i &= 0 \quad (V = 0) \\ 0.004 V_L + 2 \text{ k} \cdot i &= 0 \end{aligned} \right\} \rightarrow R_N = \frac{V}{i} = 50 \text{ [k}\Omega\text{]}$$

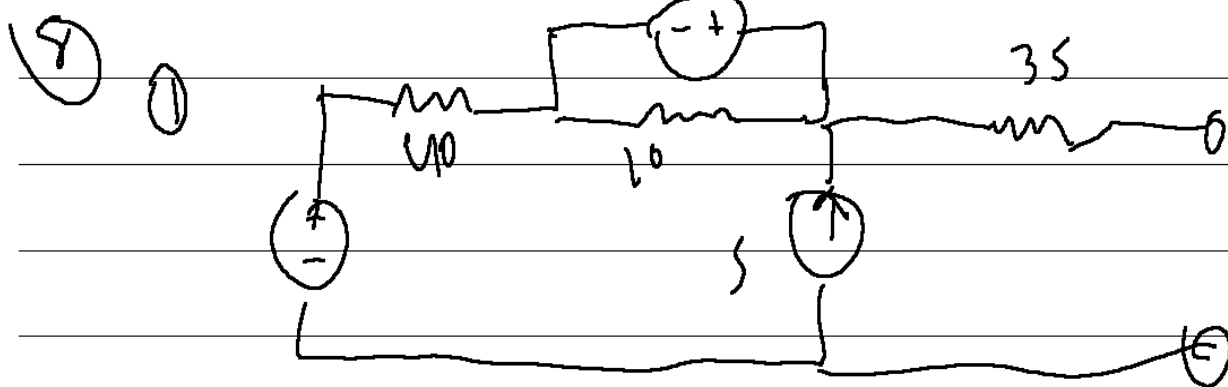
$$\textcircled{4} P_L = \frac{V_{th}^2}{4R_{th}} = \frac{(-625)^2}{4 \times 50 \text{ k}} = \text{--- [W]}$$




$$V_s = 30 \times 40 = 1,200$$

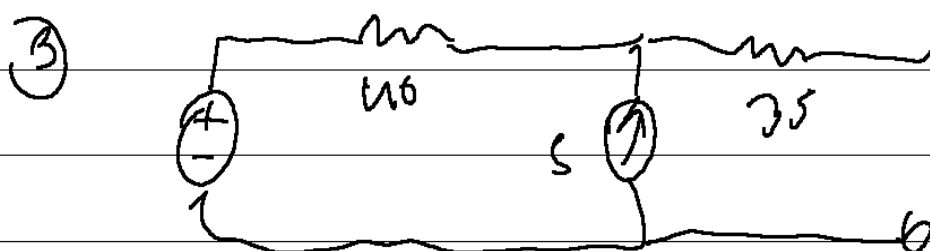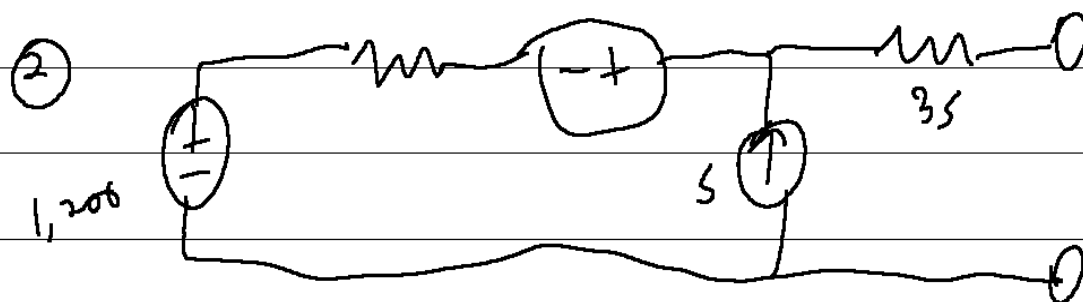

$$V_s = 1,200 + 130 = 1,350$$

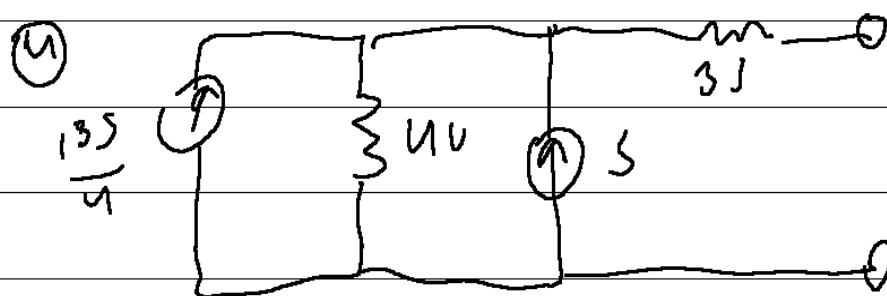


$$i_s = 1,350 / 40 = 135/4$$

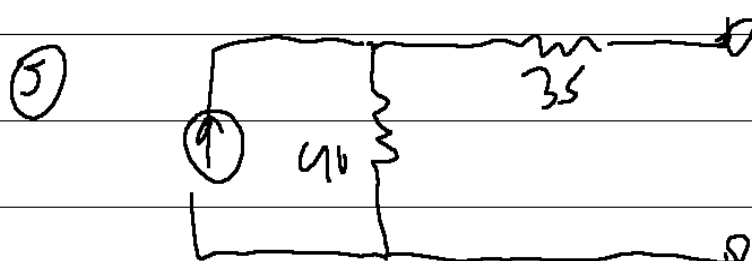

$$i_s = \frac{135}{4} + 5 = \frac{155}{4}$$

⑥

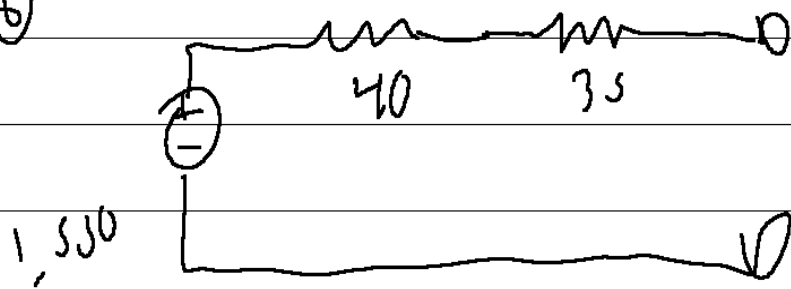


$$V_s = \frac{1.55}{4} \times 40 = 1.550$$

$$R_s = 40 + 3 = 43$$

Test


⑦

①

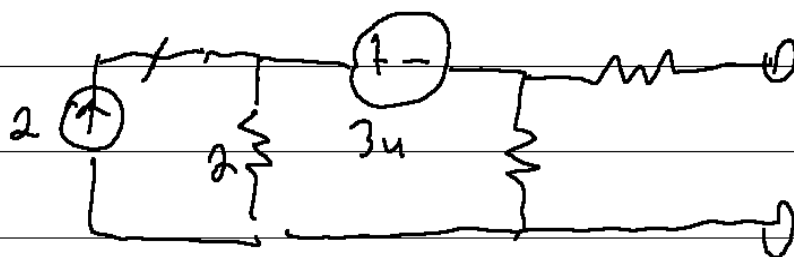


(ignore R_s)


②

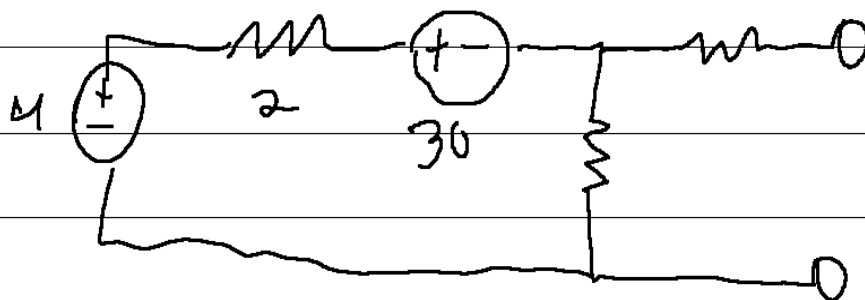


③

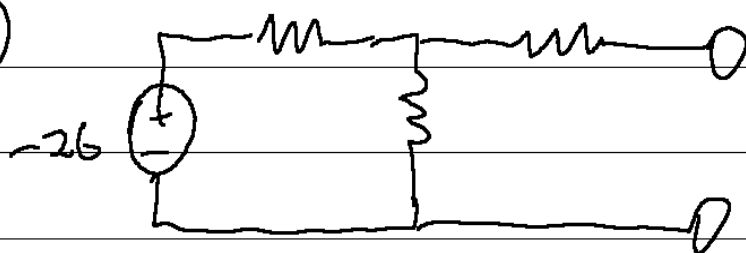


④

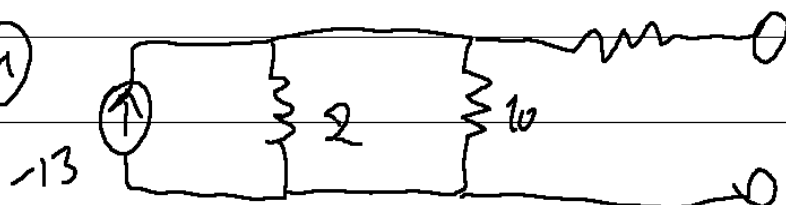


⑤

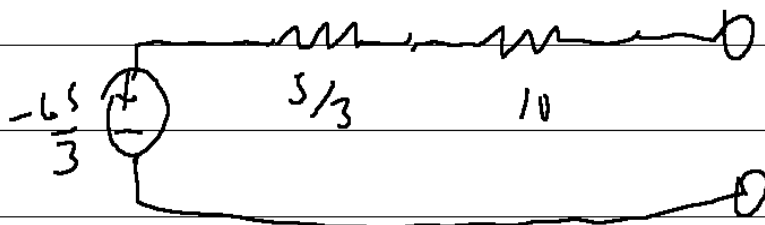

⑤

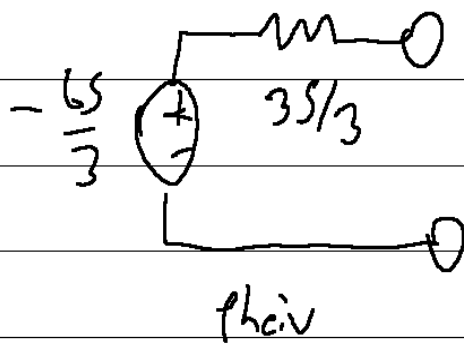


⑤'

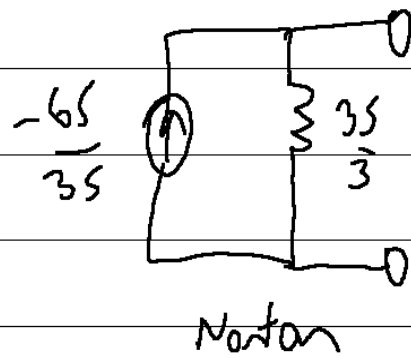

⑥

①

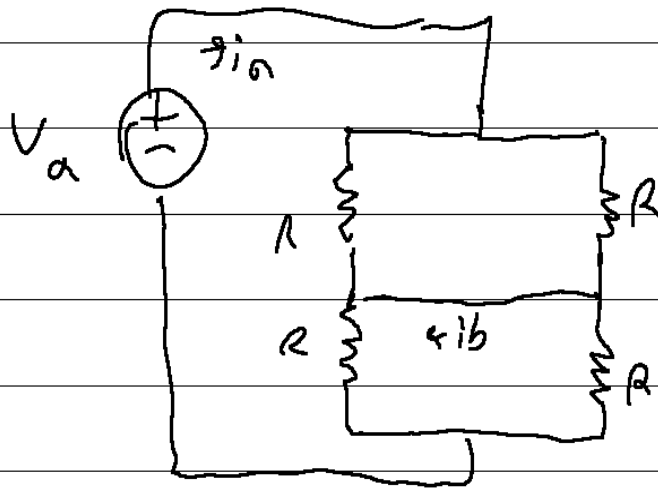


$$i_a = \frac{V_a}{(R // 2R)} = \frac{V_a}{R}$$

$$i_b = 0$$

$$i_c = -\frac{V_a}{2R}$$

②

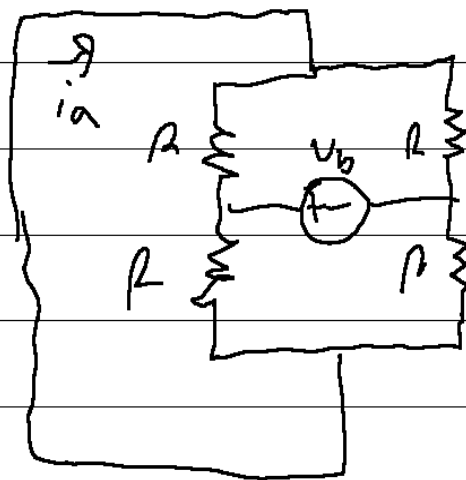

$$③ \quad i_a = V_a/R, \quad i_b = V_b/R, \quad i_c = \frac{V_b - V_a}{R}$$

③

① V_a : KVL

$$-V_a + 40i_a + 1(i_a + 4i_a) = 0 \rightarrow i_a = \frac{V_a}{50}$$

KVL

$$40i_b + 1(i_a + 9i_a) = 0 \rightarrow i_b = 0$$

$$\rightarrow V_o = 20(9i_a + 9i_b) = \underline{-\frac{18}{5}V_a}$$

② V_b :

$$③ V_o = -\frac{18}{5}V_a - \frac{18}{5}V_b$$

④ ① Supermesh 1+2+3 (KVL)

$$-27 - V_x + 2i_y + i_3 \left(\frac{1}{6}\right) = 0$$

$$(i_y = i_1, V_x = -i_1/5)$$

② Supermesh 1+2 (KVL)


$$i_1 - i_2 = -10$$

③ Supermesh 2+3 (KVL)

$$i_2 - i_3 = -2V_x$$

$$\begin{bmatrix} 11/5 & 0 & 1/6 \\ -1 & 1 & 0 \\ -2/5 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 27 \\ 10 \\ 0 \end{bmatrix}$$

③

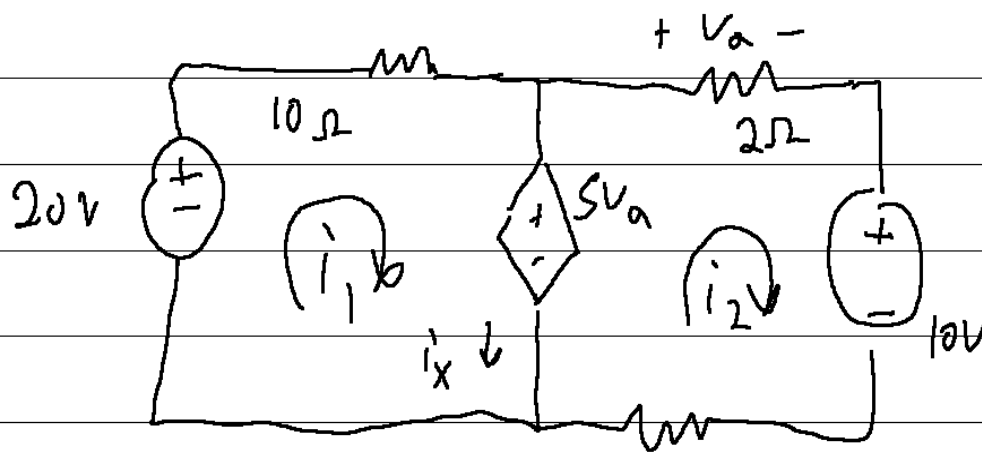

$$\left(\begin{array}{l} \textcircled{1} \text{ mesh 1 (KVL)} \\ -20 + 10i_1 + 5V_a = 0 \quad (V_a = 2i_2) \\ \textcircled{2} \text{ mesh 2 (KVL)} \\ 10 + 10i_2 - 5V_a + V_a = 0 \end{array} \right)$$

$$i_1 = 7, \quad i_2 = -5(A)$$

$$i_x = i_1 - i_2 = 12(A)$$

① node 1 (KCL)

$$20 + \underline{V_1} \cdot 10 + 5i_a = 0 \quad (i_a = 2V_2)$$

② node 2 (KCL)

$$(-5i_a + i_a) + 2V_2$$

$$\rightarrow V_1 = -7, \quad V_2 = 5(V)$$

$$\textcircled{3} \quad i_x = 5i_a - i_a = 40(A)$$

②

① Supernode 1+2+3 (KVL):
 $-27 + i_x + 2V_y + v_3/6$
 $(V_y = v_1, i_x = v_1/5)$

②

Supernode 1+2 (KVL):
 $v_1 - v_2 = -10$

③


Supernode 2+3 (KVL):
 $v_2 - v_3 = -2i_x$

$$\rightarrow \begin{bmatrix} 1/5 & 0 & 1/6 \\ -1 & 1 & 0 \\ -2/5 & -1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 27 \\ 10 \\ 0 \end{bmatrix}$$

7.4 Singularity functions

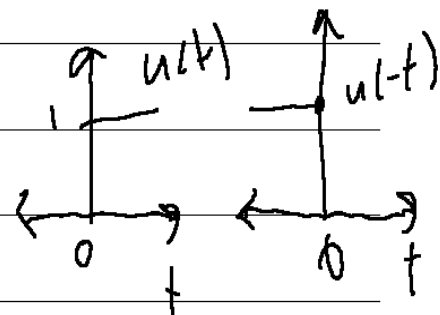
(1) Unit step ft. $u(t)$

① Definition $u(t) \begin{cases} = 0 & (t < 0) \\ = 1 & (t \geq 0) \end{cases}$



② Shifted/multiplied $u(t)$:
 $V_s u(t - t_0)$

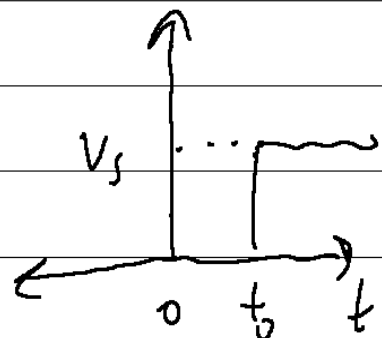③ Unit pulse ft. $\pi(t)$:
 $\pi(t) = u(t + \frac{1}{2}) - u(t - \frac{1}{2})$




(2) Unit ramp ft. $r(t)$

① Definition:

$$r(t) \begin{cases} = 0 & (t \leq 0) \\ = t & (t \geq 0) \end{cases}$$


$$= t \cdot u(t) = t [t \geq 0]$$

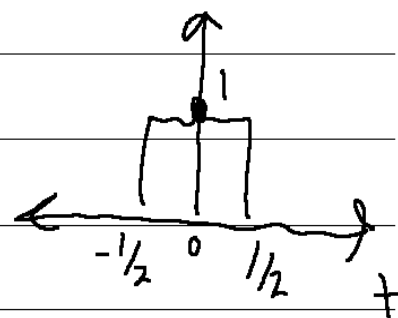

② Shifted multiplied $r(t)$

$$V_s \cdot r(t - t_0) = V_s (t - t_0) \cdot u(t - t_0)$$


$$= V_s (t - t_0) [t \geq 0]$$

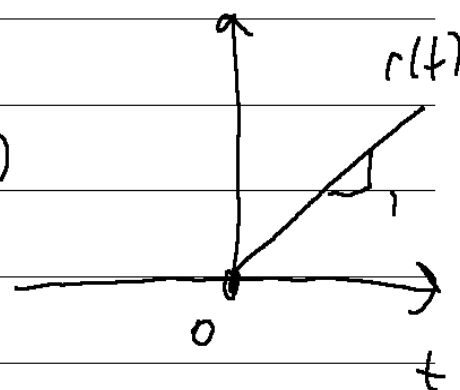

③ integ/diff

$$\frac{dr(t)}{dt} = u(t)$$
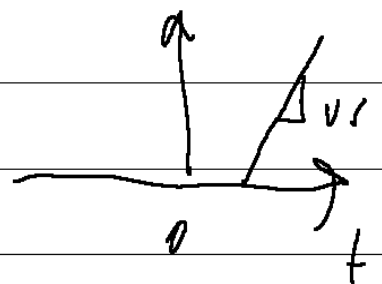
$$\int_{-\infty}^t u(\lambda) d\lambda = t \cdot u(t) = r(t)$$



Circuits Test #2 Recap

1a) Supernode 1+2

$$\textcircled{1} \text{ KCL: } \frac{V_1}{10} + \frac{(V_1 - V_4)}{2} + \frac{V_2}{20} + \frac{-V_x}{2} = 0 \quad (-V_x = V_2 - V_3)$$

$$\rightarrow 12V_1 + 11V_2 - 10V_3 - 10V_4 = 0$$

$$\textcircled{2} \text{ KVL: } V_1 - V_2 = 10$$

$$\begin{pmatrix} 12 & 11 & -10 & -10 \\ -1 & 1 & 0 & 0 \\ \hline 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$

$$\begin{bmatrix} 12 & 11 & -10 & -10 \\ 1 & -1 & 0 & 0 \\ \hline n/a & n/a & n/a & n/a \\ n/a & n/a & n/a & n/a \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \\ n/a \\ n/a \end{bmatrix}$$

1b)

$$\textcircled{1} \text{ KVL: } 20(i_2 - i_1) - V_x + 40 + 40 = 0, \quad -V_x = 2(i_2 - i_4)$$





$$\rightarrow -20i_1 + 22i_2 - 2i_4 = -140$$

$$\textcircled{2} \text{ KCL: } i_2 - i_3 = -2V_x \quad V_x = 2(i_4 - i_2)$$


$$\rightarrow -3i_2 - i_3 + 4i_4 = 0$$

$$\begin{bmatrix} -20 & 22 & 0 & -2 \\ 0 & -3 & -1 & 4 \\ \hline n/a & n/a & n/a & n/a \\ n/a & n/a & n/a & n/a \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} -140 \\ 0 \\ n/a \\ n/a \end{bmatrix}$$

2)

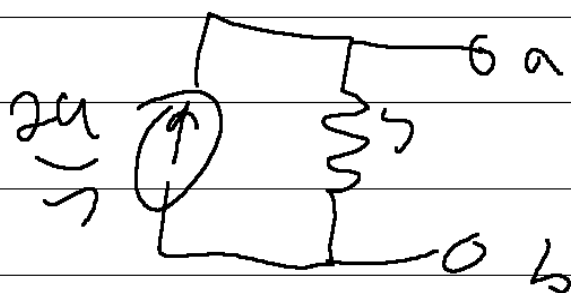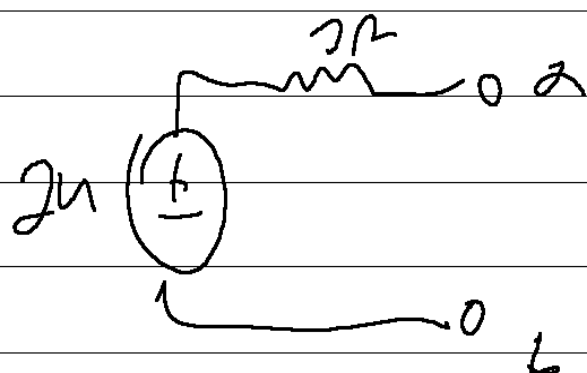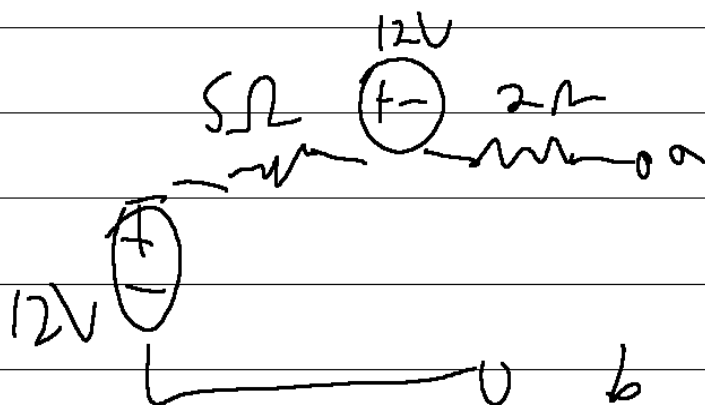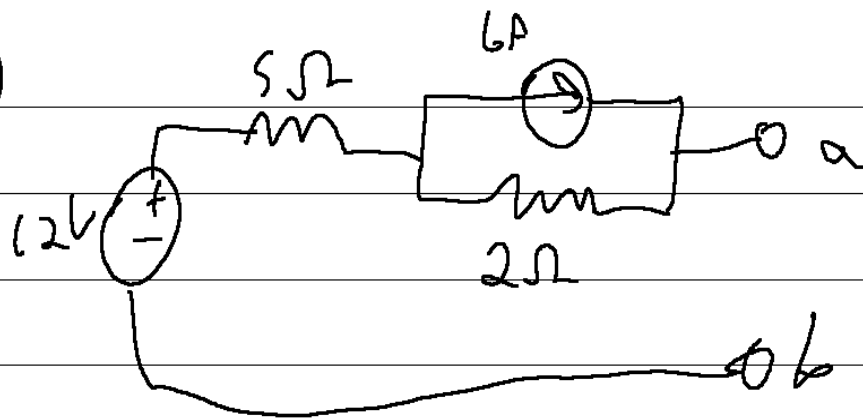

3a)

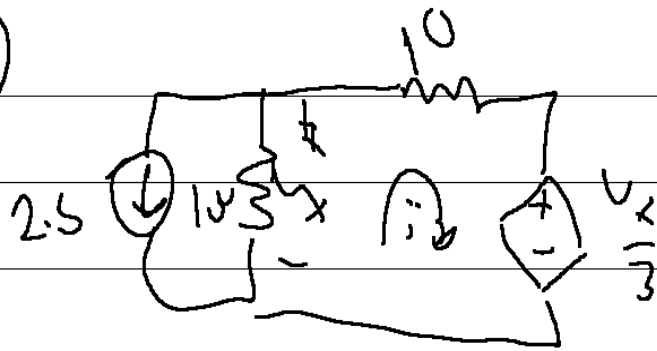

$$(KVL) \quad 2.5 + \frac{V_x}{10} + \frac{(V_x - \frac{V_x}{3})}{10} = 0$$

$$\Rightarrow V_x = -15(V)$$


or

$$(KVL) \quad (-V_x + 10 + \frac{V_x}{3}) = 0$$

$$V_x = -10(1 + 2/3)$$

$$\Rightarrow V_x = -15$$

3b)

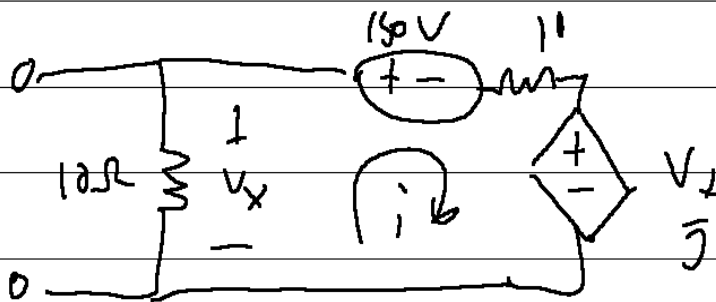

$$(KVL) \quad \frac{V_x}{10} + \frac{(V_x - 150) - \frac{V_x}{3}}{10} = 0$$

$$\Rightarrow V_x = 90(V)$$

or

$$(KVL) \quad \frac{V_x}{10} + \frac{(V_x - 150) - \frac{V_x}{3}}{10} = 0$$

$$\Rightarrow V_x = \underline{90(V)}$$

(KVL)

$$(-V_x + 150 + 10 + \frac{V_x}{3}) = 0$$

$$V_x = -10 \Rightarrow V_x = 90$$

3c)

$$V_x = 90 - 15 = \underline{75(V)}$$

V_a

$$(1\text{KVL}) \quad -80 - 80 \times 2 + 40 \times 0 + V_{oc} = 0$$

$$\rightarrow V_{oc} = 240\text{V}$$

or

$$(1\text{KCL}) \quad \frac{V_{oc} - 80}{80} - 2 + 0 = 0$$

$$\rightarrow V_{oc} = 240\text{V}$$


$$(1\text{KVL}) \quad -80 + 80(i_{sc} - 2) + 40i_{sc} = 0$$

$$\rightarrow i_{sc} = \underline{2\text{A}}$$

or

$$(1\text{KCL}) \quad \frac{V - 80}{80} - 2 + i_{sc} = 0, \quad V = 40i_{sc}$$

$$\rightarrow i_{sc} = 2\text{A}$$

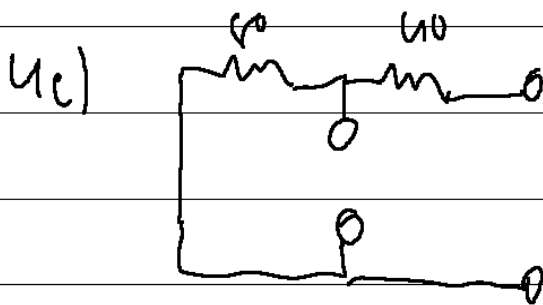

$$R_{th} (= R_N) = 80 + 40 = \underline{120\Omega}$$

$$(1d) \quad P_L = \frac{V_{th}^2}{4R_{th}} = \frac{240^2}{4 \times 120} = \underline{120\text{W}}$$

$$\left(\frac{V_s^2}{4R_L} \right)$$

Final:

1) General Concepts

2) Mesh Current

3) Node Voltage Matrix

4) Superposition

5) Source Transformation

6) Thévenin Norton


·
· } Upcoming
·
·

13) Unit impulse $f(t)$, $\delta(t)$

① Definition:

$$\delta(t) = 0 \quad (t \neq 0)$$

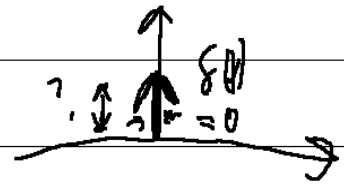
$$\int_{-\infty}^{\infty} \delta(t) dt = 1 \quad (\delta(t) \neq 1: \text{unit area, strength})$$



② Sifting / Sampling $f(t)$:

$$\int_{-\infty}^{\infty} f(t) \delta(t) dt = f(0)$$

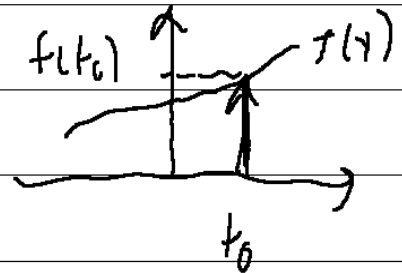
$$\int_{-\infty}^{\infty} f(t) \delta(t - t_0) dt = f(t_0)$$




③ integ / diff:

$$\frac{du(t)}{dt} = \delta(t)$$
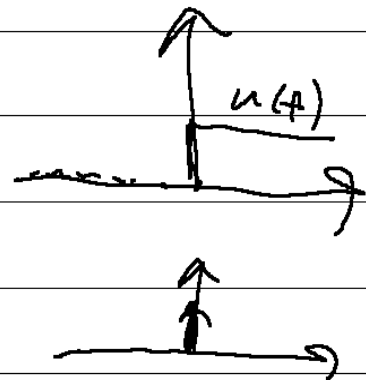
$$\int_{-\infty}^t \delta(\lambda) d\lambda = u(t)$$



11.2 Instantaneous and Average Power

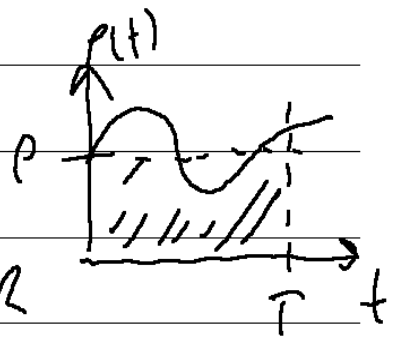

(1) Instantaneous power

$$p(t) = i(t)v(t) = v^2(t)/R = i^2(t)R$$

(2) Average power (AC component)

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{v^2(t)}{R} dt = \frac{1}{R} \frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt$$

$$\frac{V_{rms}^2}{R} \quad (\text{OR} \quad \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt = R \cdot I_{rms}^2)$$

11.4 RMS (root mean square)

(1) "Effective" Value

$$V_{rms} (= V_{eff}) = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$$

$$I_{rms} (= I_{eff}) = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

(2) Sinusoidal signals

$$V_m \cos(\omega t): \quad V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_m^2 \cos^2 \omega t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T V_m^2 \frac{(1 + \cos 2\omega t)}{2} dt} = \frac{V_m}{\sqrt{2}}$$

(OR $V_{rms}^2 = \frac{V_m^2}{2}$)


Power Superposition

(1) Orthogonality

① Avg of the product of two fts is zero

② Sin & cos satisfy the orthogonality with 3 conditions

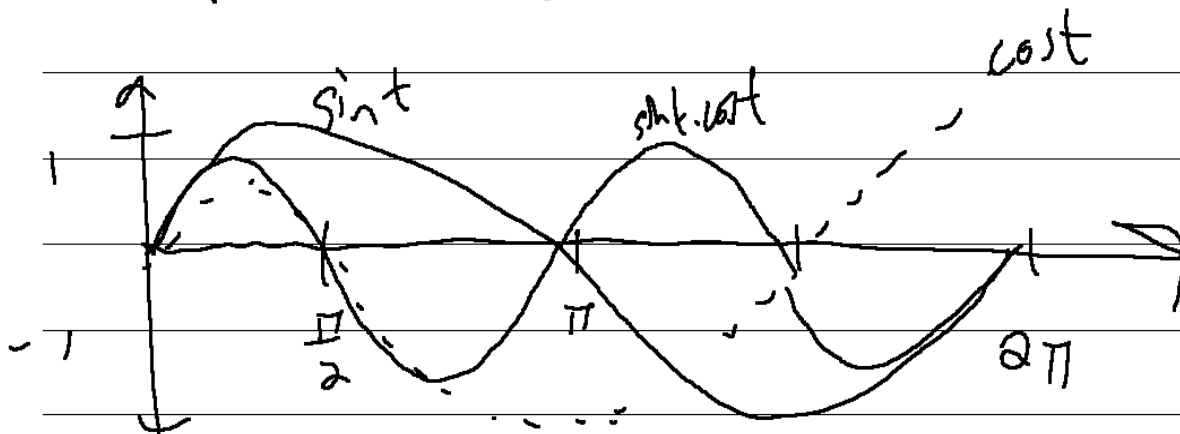(sin & cos of same freq/phase are orthogonal
cos is orthogonal to sin & cos of different freq.
sin is orthogonal to sin & cos of different freq.



(2) RMS Superposition (orthogonal signals)

$$\begin{aligned} \textcircled{1} V_{rms}^2 &= \frac{1}{T} \int_0^T [V_1(t) + V_2(t)]^2 dt = \frac{1}{T} \int_0^T V_1^2 dt + \frac{1}{T} \int_0^T V_2^2 dt \\ &\quad + \frac{1}{T} \int_0^T 2V_1 V_2 dt = V_{rms,1}^2 + V_{rms,2}^2 \end{aligned}$$

$$\begin{aligned} \textcircled{2} \text{Generalization: } V_{rms}^2 &= V_{rms,1}^2 + V_{rms,2}^2 + \dots \\ &= \sum_{n=1}^N V_{rms,n}^2 \quad (n: \text{integer}) \end{aligned}$$


③ Avg power from N orthogonal signals:

$$P = \frac{1}{R} V_{rms}^2 = \frac{1}{R} \sum_{n=1}^N V_{rms,n}^2 = \sum_{n=1}^N P_n$$

6.2 Capacitance

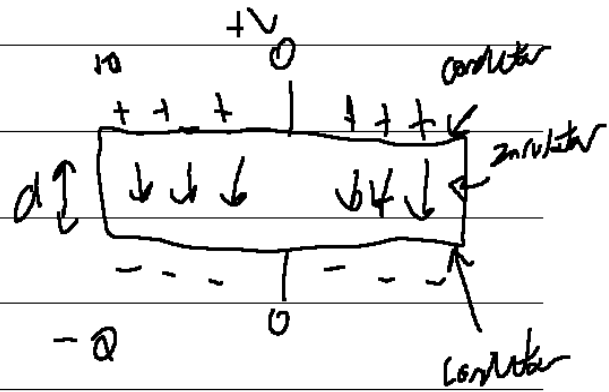(1) Capacitor

① A device to store energy in the form of electric field




② Capacitance C :

Capacity of charge storage [Farad = coulomb/volt]

$$Q = (C \text{ or } q(t)) = C \cdot V(t) \quad \left(C = \frac{\epsilon A}{d}, \quad \epsilon = \text{dielectricity}, \quad A = \text{area}, \quad d = \text{distance} \right)$$

③ Displacement current
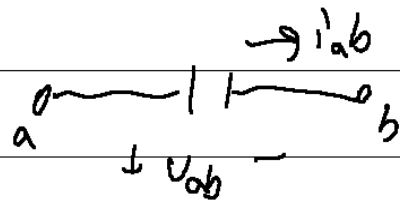
$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} (C \cdot V(t))$$





(No actual voltage crosses insulator.)

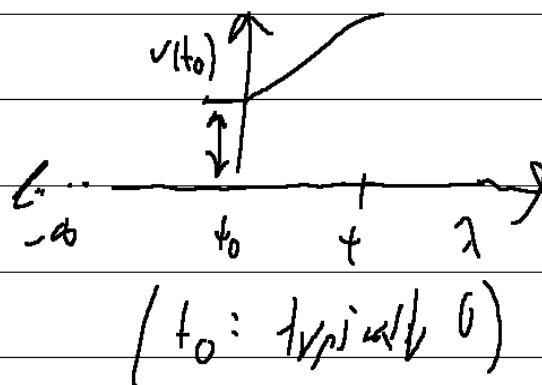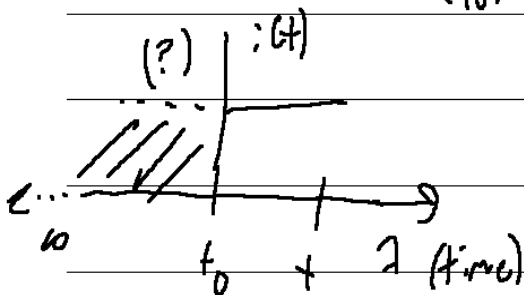(2) Initial condition $v(t_0)$

$$(1) \quad v(t) = \frac{1}{C} \int_{t_1}^{t_2} i(t) dt = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$= \underbrace{\frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau}_{v(t_0)} + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$



(3) Energy Storage


$$w(t) = \int_{-\infty}^t p(\lambda) d\lambda = \int_{-\infty}^t i(\lambda) v(\lambda) d\lambda = \frac{1}{2} C v^2(t)$$

(always positive value)

6.3 series/parallel capacitors

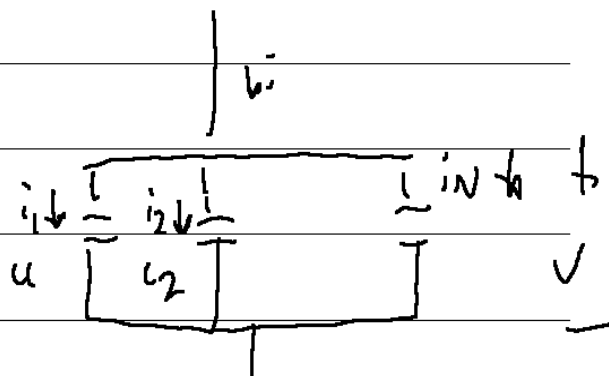
(1) Parallel

$$\begin{aligned} i &= i_1 + i_2 + \dots + i_N \\ &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt} \\ &= C_{eq} \frac{dv}{dt} \\ \rightarrow C_{eq} &= C_1 + C_2 + \dots + C_N \end{aligned}$$



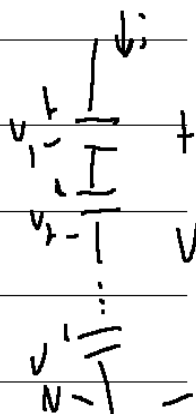(2) Series

$$\begin{aligned} v &= v_1 + v_2 + \dots + v_N \\ &= \frac{1}{C_1} \int_{t_0}^t i(\lambda) d\lambda + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\lambda) d\lambda + v_2(t_0) \\ &\quad + \dots + \frac{1}{C_N} \int_{t_0}^t i(\lambda) d\lambda + v_N(t_0) \\ &= \frac{1}{C_{eq}} \int_{t_0}^t i(\lambda) d\lambda + v(t_0) \end{aligned}$$




$$\rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

6.4 Inductance

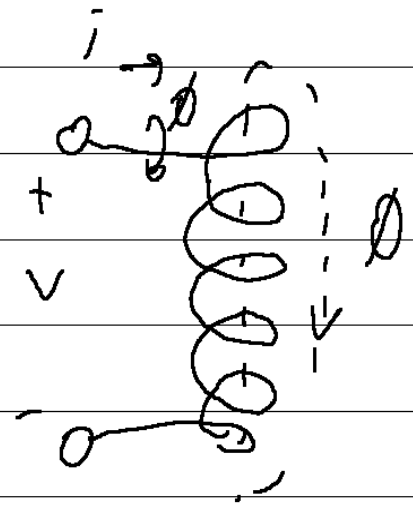(1) Inductor

- ① A device to store energy in the form of magnetic field




② Inductance L :

Capacity of magnetic field induction [Henry = $\text{Wb} \cdot \text{sec} / \text{Amp}$]

$$L = \frac{N\Phi}{i} \quad (\Phi: \text{magnetic field intensity}, N: \# \text{ of coil turn})$$

③ Faraday's Law

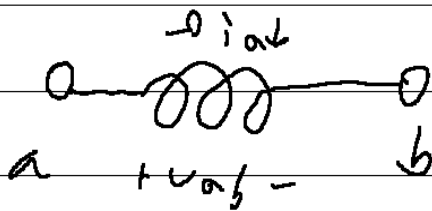
$$v(t) = N \frac{d\Phi(t)}{dt} = \frac{d}{dt} \left(\frac{N\Phi}{i} \right) = L \frac{di(t)}{dt}$$




A1 Exponential ft.

(1) Decay constant, τ

$$v(t) = V_0 e^{-t/\tau}$$

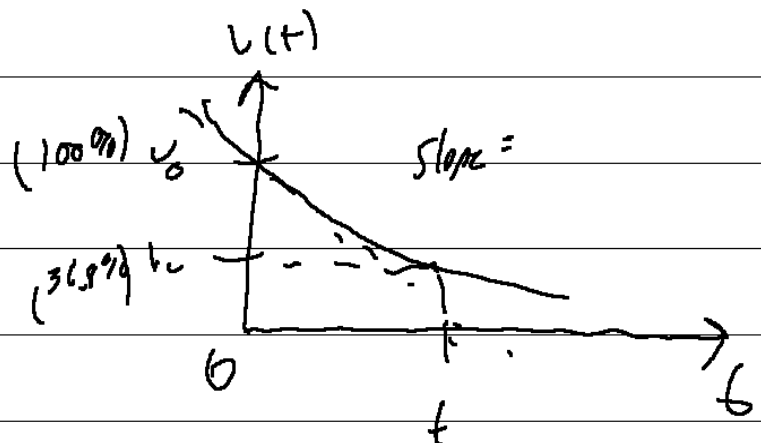

(2) Realization of constant ft.

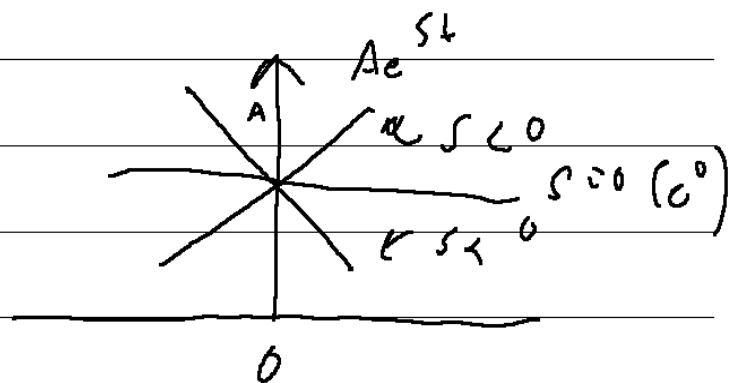

(3) Multiplication analogy of differentiation
("s - operator")

$$\textcircled{1} \frac{d}{dt} (Ae^{st}) = s(Ae^{st})$$

\textcircled{2} diff of expon ft is "equiv" to multiplication by s

$$\textcircled{3} \frac{1}{dt} e^{(q+1)st} = \frac{d}{dt} e^{st} = s e^t$$

Chapter 7 First-Order Circuits

7.2 Source-free RL

(1) diff eq

① (KCL) $L \frac{dv(t)}{dt} + \frac{v}{R} = 0 \quad (t > 0)$

$$\frac{dv}{dt} + \frac{v}{R_L} = 0$$

$$\frac{dv}{v} = - \frac{dt}{R_L}$$

$$\int_{v(0)}^{v(t)} \frac{dv}{v} = - \frac{1}{R_L} \int_0^t dt$$

$$\ln v(t) - \ln v(0) = - \frac{t}{R_L}$$



$$\ln \frac{v(t)}{v(0)} = - \frac{t}{R_L}$$

$$\ln \frac{v(t)}{v(0)} = - \frac{t}{R_L}$$

$$\frac{v(t)}{v(0)} = e^{-t/R_L} \quad (t > 0)$$

② Natural response: $v(t) = v(0) e^{-t/R_L} = V_0 e^{-t/R_L}$

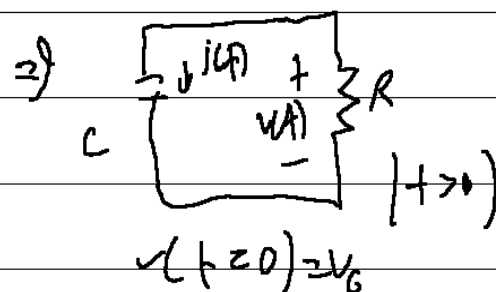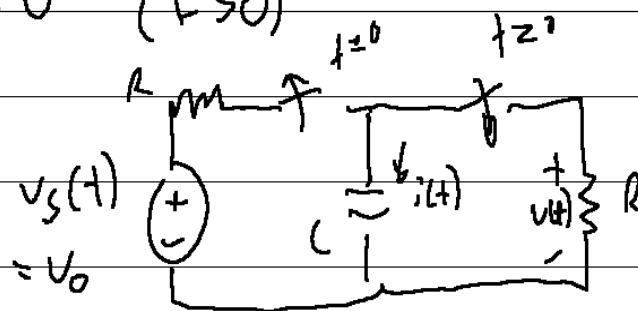General form: $v(t) = K e^{st} \quad (t > 0) \quad (s = -\frac{1}{R_L} = -\frac{1}{\tau})$




(2) capacitor behavior

① initial condition:

$$v(0^-) = v(0^+) = v(0) = K = (-V_0) \leftarrow \dots$$

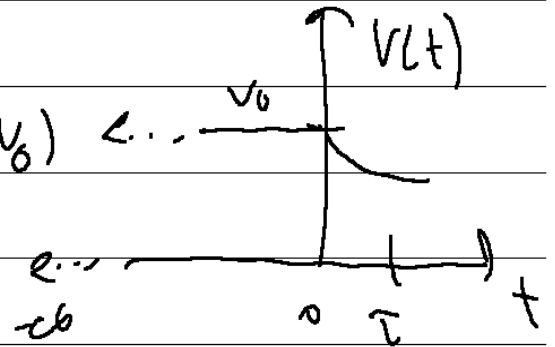
($\because C \frac{dv}{dt} \neq \infty$; capacitor voltage)



(2) capacitor behavior

① initial condition:

$$v(0^-) = v(0^+) = v(0) = K (=V_0)$$

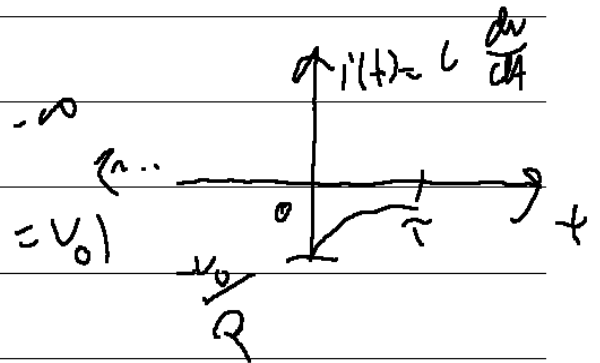


② $i(0^-) \neq i(0^+) = i(0)$

$i = 0$ (open-circuit) with a const. voltage for a very long time.

7.3 Source-free RL

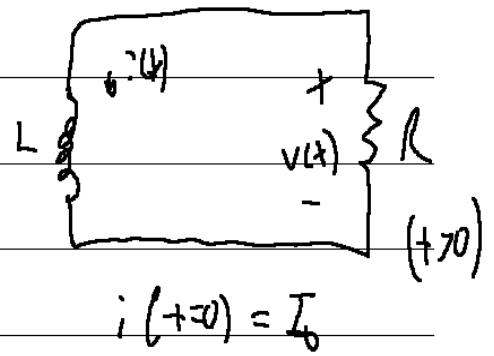(1) diff eq

① (KVL) $L \frac{di(t)}{dt} + iR = 0 \quad (t > 0)$



$$\frac{di}{dt} + \frac{R}{L} i = 0$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\int_{i(0)}^{i(t)} \frac{di}{i} = -\frac{R}{L} \int_0^t dt$$

$$\ln i(t) - \ln i(0) = -\frac{R}{L} t$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} t$$



$$\frac{i(t)}{i(0)} = e^{-\frac{R}{L} t} \quad (t > 0)$$

② Natural response: $i(t) = i(0) e^{-\frac{R}{L} t} = I_0 e^{-\frac{R}{L} t}$

General form: $i(t) = I_0 e^{st} \quad (t > 0) \quad (s = -\frac{R}{L} = -\frac{1}{\tau})$


(2) Inductor Behavior

① initial condition:

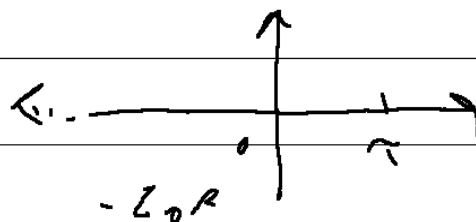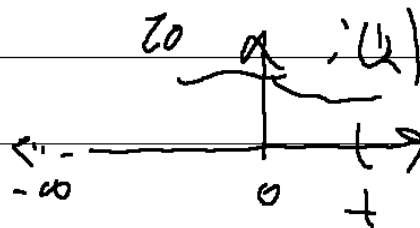


(7) "s-operator" approach

① (KVL)

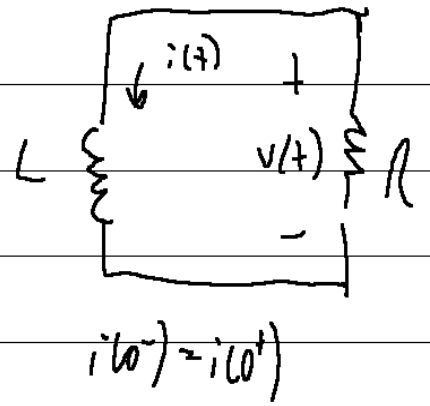

Sample Test #3 - Answers

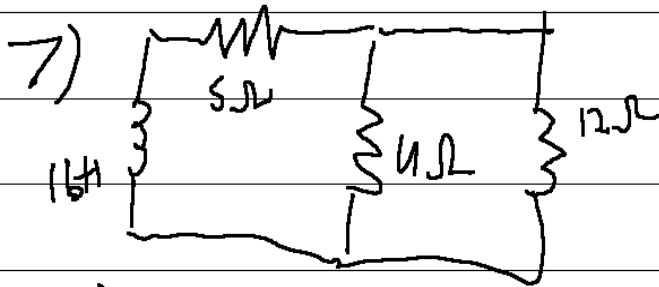


$$i(0^-) = i(0^+) = 16 \text{ (A)}$$

① $i(t) = ?$ ② $v(t) = ?$ ($t > 0$)

③ $\tau = ?$

$$v = L \frac{di}{dt}$$

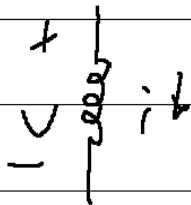

① (KVL) $16 \frac{di}{dt} + 5i + (4/12) \cdot 0 = 0$

$$\frac{di}{dt} + \frac{1}{2}i = 0$$

$$s_i + \frac{1}{2} = 0 \quad (s = -\frac{1}{2})$$


$$i(0) = 16 e^{-\frac{1}{2}t} \text{ A}$$

$$K e^0 = 16 \quad (K = 16)$$

$$\rightarrow i(t) = 16 e^{-\frac{1}{2}t} \text{ [A]} \quad (t > 0)$$

② $v(t) = -L \frac{di}{dt} = 128 e^{-\frac{1}{2}t} \text{ [V]} \quad (t > 0)$

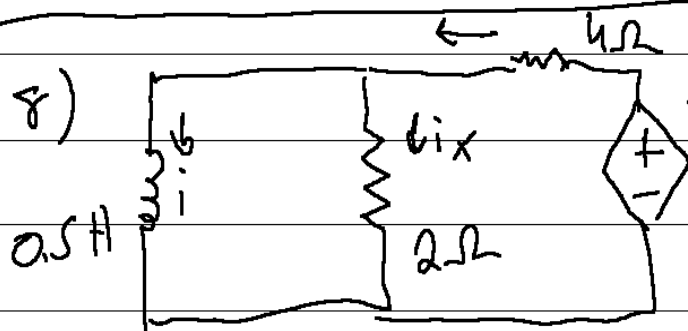③ $L_{eq} = 16$, $R_{eq} = 5 + (4/12) = 8 \frac{2}{3}$
 $\tau = \frac{L_{eq}}{R_{eq}} = 2 \text{ (sec)}$



$$i(0^-) = i(0^+) = 10 \text{ (A)}$$

① $i(t) = ?$ ($t > 0$) ② $R_{eq} = ?$


① (KVL) $0.5 \frac{di}{dt} - 2i_x = 0$
 (KVL) $2i_x - 3i + 4(i_x) = 0$

$$0.5 \frac{di}{dt} + \frac{1}{3}i = 0$$

$$\frac{di}{dt} + \frac{2}{3}i = 0$$



$$s_i + \frac{2}{3} = 0 \quad (s = -\frac{2}{3})$$

OR

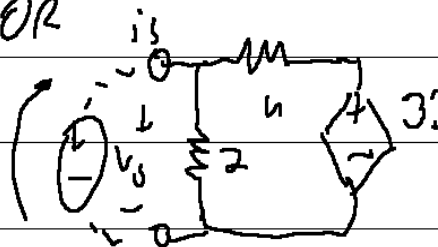

$$i(0) = K e^0 = 10 \rightarrow i(t) = 10 e^{-\frac{2}{3}t} \text{ [A]} \quad (t > 0)$$

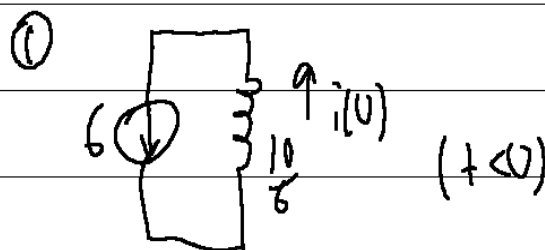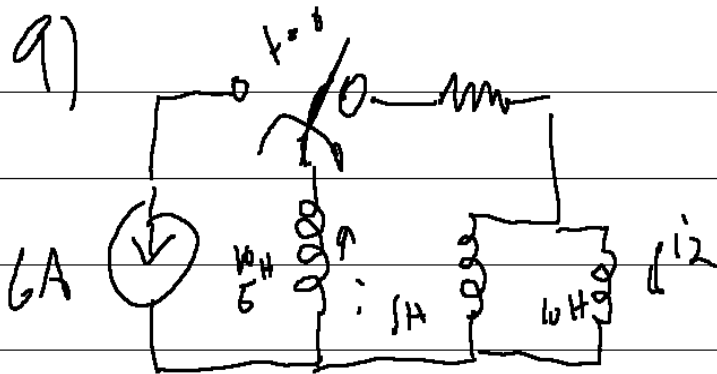② $\tau = \frac{3}{2} \text{ [sec]} \rightarrow \begin{cases} R_{eq} = 1 \frac{1}{3} \text{ (}\Omega\text{)} \\ L_{eq} = 0.5 \text{ [H]} \end{cases}$



$$\underline{i(0^-) = 6 = i(0^+) \quad (A)}$$

① $i(0^-) = i(0^+) = ?$


② $i_1(t) = ?$ ③ $i_2(t) = ? \quad (t > 0)$

④ $\tau = ?$

↻

$$L_{eq} = \frac{10}{6} + (5 // 10) = 5H$$

$$R_{eq} = 20 \Omega$$

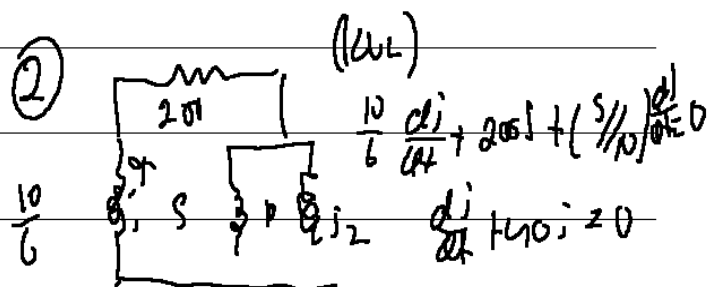


$$(t > 0) \quad 5i_1 + 4i_2 = 0 \quad (i_2 = -4i_1)$$

$$i_1(0) = i_2(0) = 6 \rightarrow i_1(t) = 6e^{-40t} [A] \quad (t > 0)$$

③ $i_2(t) = \left(\frac{\frac{10}{6}}{\frac{1}{5} + \frac{1}{10}} \right) i_1(t) =$


$$\underline{2e^{-40t} [A] \quad (t > 0)}$$

47)

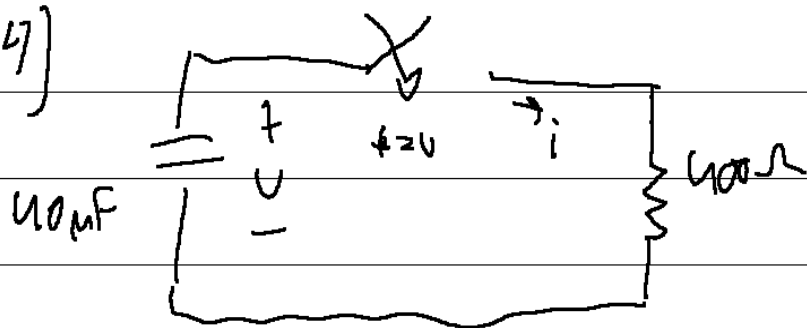

$$V(0^-) = V(0^+) = 100 \text{ [V]}$$

① $V(t) = ?$ ② $i(t) = ?$ ($t > 0$)

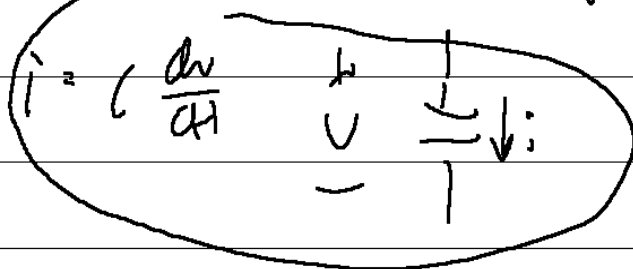

① KCL

$$40 \mu \frac{dV}{dt} + \frac{V}{400} = 0$$

$$\frac{dV}{dt} + \frac{V}{1.6 \times 10^{-2}} = 0$$


$$s + \frac{1}{1.6 \times 10^{-2}} = 0 \quad (s = -62.5)$$

$$V(t) = V e^{st} = 100 e^{-62.5t} \text{ [V]} \quad (t > 0)$$

② $i(t) = -\left(\frac{dV}{dt}\right) = 0.216 e^{-62.5t} \text{ (A) (10)}$

$$L = \frac{V}{i} =$$

5)

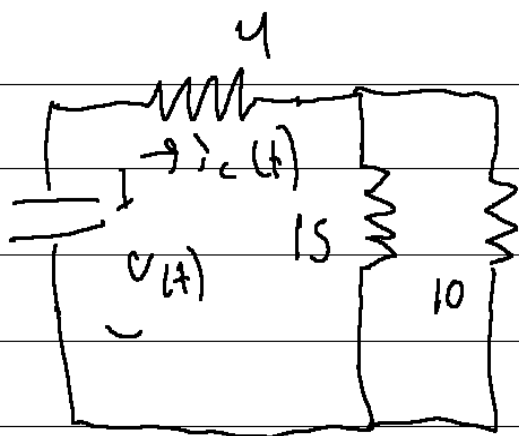


$$V(0^-) = V(0^+) = 100 \text{ [V]}$$

① $V(t)$ ② $i_c(t)$ ③ $i(t)$ ($t > 0$)

② $i_c(t) = -\left(\frac{dV}{dt}\right) = 10 e^{-2t} \text{ (A)} \quad (t > 0)$

③ $i(t) = \left(\frac{\frac{1}{10}}{\frac{1}{15} + \frac{1}{10}}\right) i_c(t) = 6 A e^{-2t} \text{ (A)}$

①

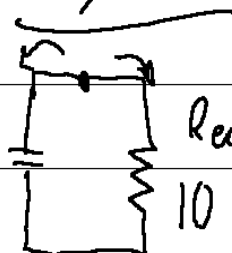

$$R_{eq} = 4 + (15 // 10) =$$



KCL $\frac{1}{20} \frac{dV}{dt} + \frac{V}{10} = 0$

$$\frac{dV}{dt} + 2V = 0$$

$$s + 2 = 0 \quad (s = -2)$$


$$V(0) = 100 \text{ (KCL 100)} \rightarrow$$
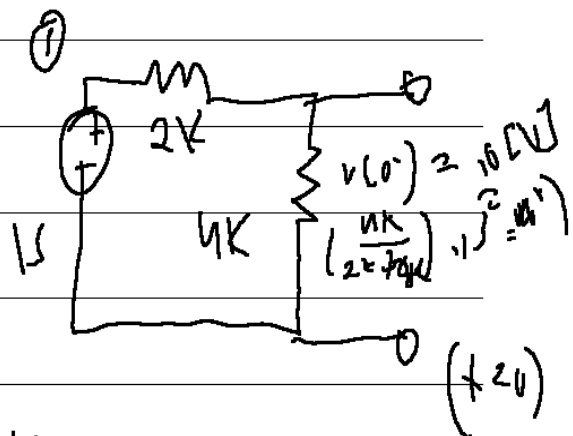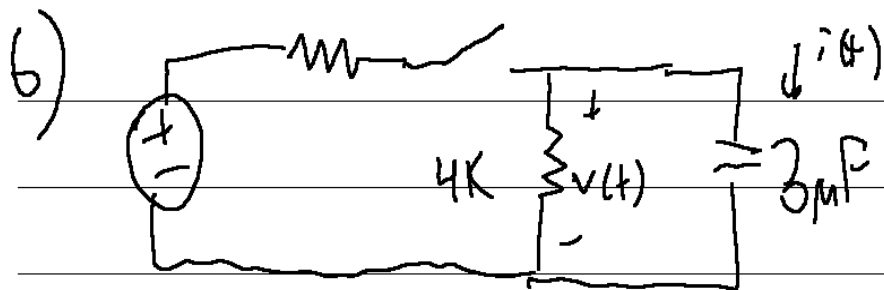
$$V(t) = 100 e^{-2t} \text{ (V)} \quad (t > 0)$$



① $v(0^-) = v(0^+) = ?$

② $v(t)$ ③ $i(t) = ?$ ($t > 0$)

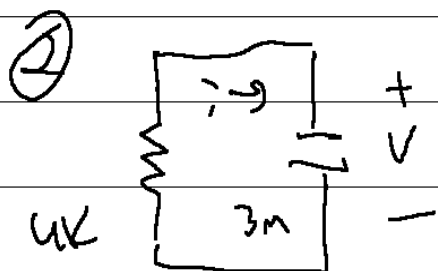

(KCL) $3m \frac{dv}{dt} + \frac{v}{4k} = 0$


(+) $\frac{dv}{dt} + \frac{v}{12} = 0$

$s + \frac{1}{12} = 0 \quad s = -\frac{1}{12}$

$v(0) = 10e^0 = 10 \rightarrow v(t) = 10 \cdot e^{-1/12 t} [V] \quad t > 0$

③ $i(t) = C \frac{dv}{dt} = -2.5m e^{-1/12 t} [A] \quad t > 0$


Test #3 Solutions

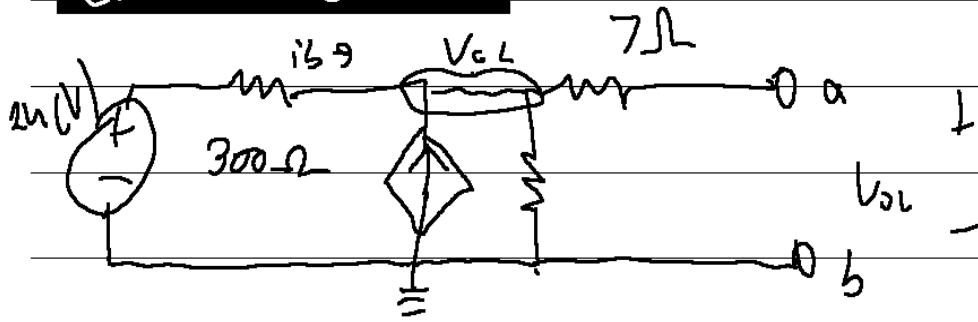

$$1a) (KCL) -i_b - 24i_b + \frac{V_{oL}}{10} = 0$$

$$\left(i_b = \frac{(24 - V_{oL})}{300} \right)$$
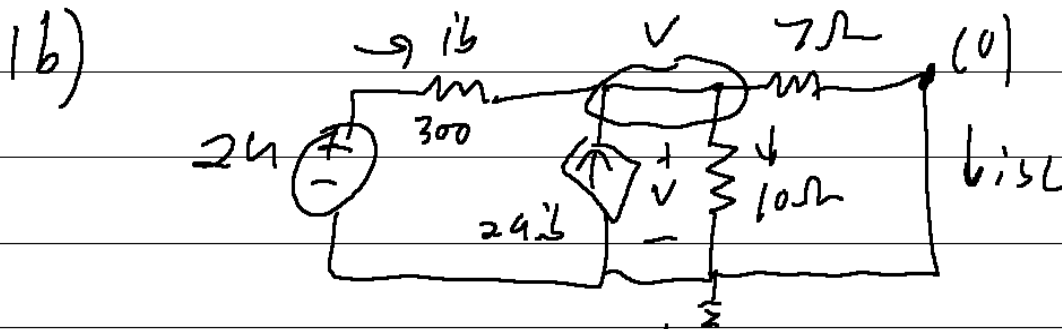
$$\rightarrow \underline{V_{oL} = 12 [V]}$$



$$(KCL) -i_b - 24i_b + \frac{V}{10} + i_{sc} = 0$$

$$\left(i_b = \frac{(24 - V)}{300} \right)$$

$$(ohm) \quad V = 7i_{sc}$$

$$\rightarrow \underline{i_{sc} = 1 [A]}$$

2)

(c) 1KΩ

$$(1\mu) \frac{d}{dt} [V(-V)] + \frac{V}{10K} = 0$$

$$(2\mu) \frac{dv}{dt} + \frac{V}{10K} = 0$$




$$\frac{dv}{dt} + \frac{V}{2 \cdot 10^{-2}} = 0$$

$$\rightarrow s + \frac{1}{2 \cdot 10^{-2}} = 0 \quad (s = -\frac{1}{2 \cdot 10^{-2}} = -50)$$

$$V(s) = K e^0 \rightarrow v(t) = 10 e^{-50t} [V] \quad (t > 0)$$

$$d) \quad i(t) = \frac{-v(t)}{R} = \frac{-10 e^{-50t}}{10K} [A] \quad (t > 0)$$
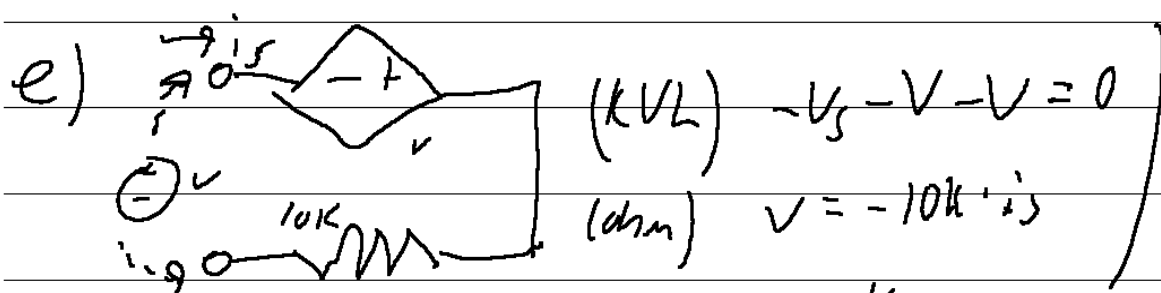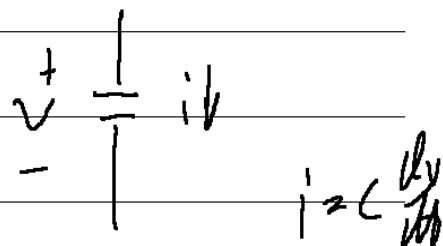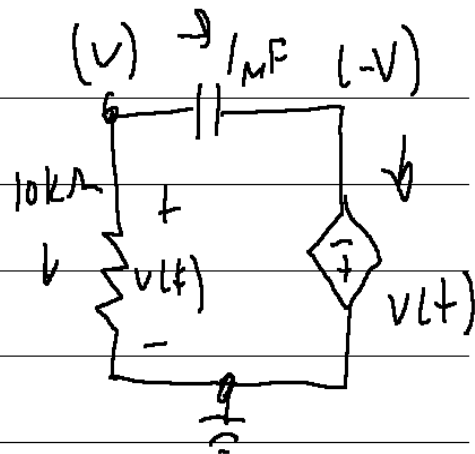
$$(or = \frac{d}{dt}(2V) = \underline{\underline{\quad}})$$



$$(KVL) -V_s - V - V = 0$$

$$(Ohm) \quad V = -10K \cdot i_s$$


$$\rightarrow R_{eq} = \frac{V_s}{I_s} = 20[K\Omega]$$

$$R_{eq} = \frac{V_s}{I_s}$$

$$\tau = C_{eq} \cdot R_{eq} = 1\mu \cdot 20K = 2 \cdot 10^{-2} [sec]$$


3)

a)

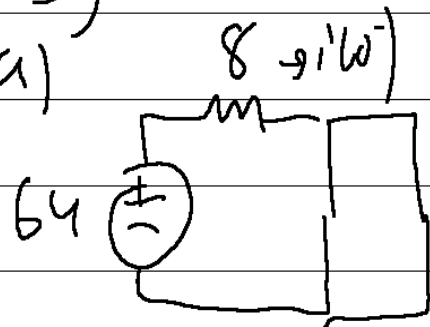


$$i'(0^-) = \frac{64}{8} = 8 \text{ A} = i'(0^+)$$

$$v = L \frac{di}{dt}$$

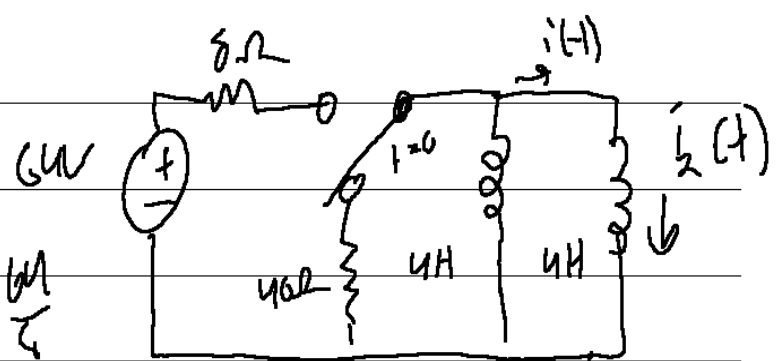

b)

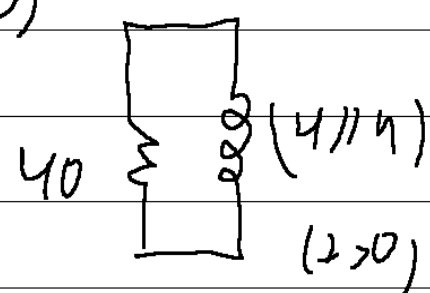

$$(4 \parallel 4) \frac{di}{dt} + 40i = 0$$

$$\frac{di}{dt} + 20i = 0$$

$$s + 20 = 0 \quad (s = -20)$$

$$i(0) = Ke^0 = 8 \rightarrow \underline{i(t) = 8e^{-20t} \text{ [A]} \quad (t > 0)}$$


$$c) \quad i_2(t) = \left(\frac{1/4}{1/4 + 1/4} \right) i(t) = 4e^{-20t} \text{ [A]} \quad (t > 0)$$

$$d) \quad v(t) = L \frac{di}{dt} = (4 \parallel 4) \frac{d}{dt} (8e^{-20t})$$

$$= -320e^{-20t} \text{ (A)} \quad t > 0$$

OR

$$-16A = \dots$$

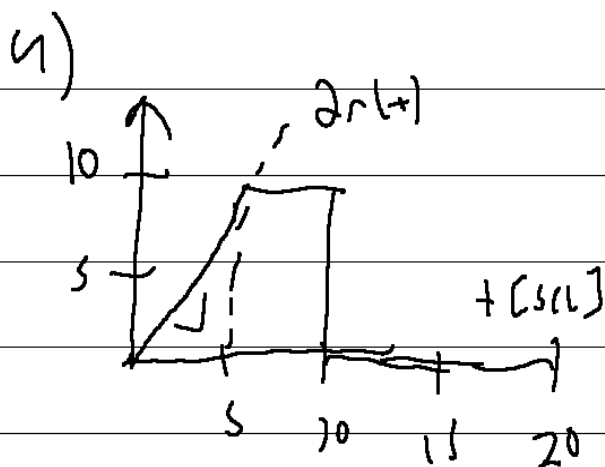

a) $i(t) = 2r(t) = 2r(t-5) = 10u(t-10) \text{ [A]}$


b)
$$I_{\text{eff}} = \frac{1}{T} \int_0^T i(t) dt = \frac{1}{15} \left[\int_0^5 2t dt + \int_5^{10} 10 dt \right] = 5 \text{ [A]}$$

c)
$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt} = \sqrt{\frac{1}{15} \left[\int_0^5 (2t)^2 dt + \int_5^{10} 10^2 dt \right]} = 6.67 \text{ [A]}$$

A2 - Complex Numbers

(1) Real numbers:

1-D system (linear) $\begin{cases} |x-1| = -1 \\ |x-1| = 1 \end{cases}$

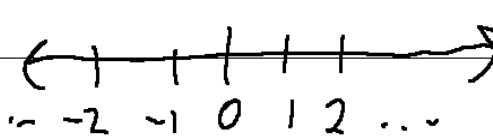


(2) Imaginary Numbers:

$$(j+1)^2 = -1 \quad \text{or} \quad j^2 = -1$$

2-D system (circular)

$$\begin{cases} |x; 1| = j \\ j |x; 1| = -1 \\ -1 |x; 1| = -j \\ -j |x; 1| = 1 \end{cases}$$

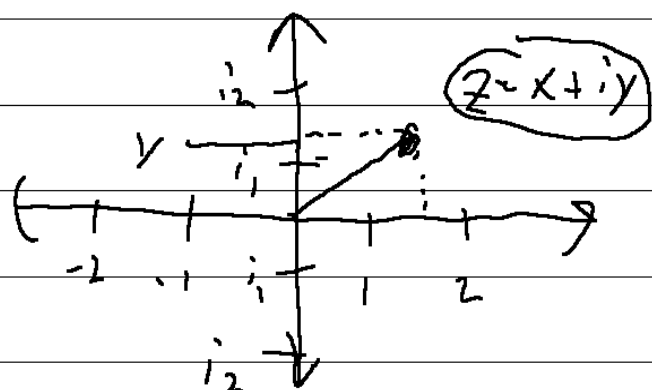

(3) Complex numbers:

$$z = x + jy \rightarrow \begin{cases} |z| = \sqrt{x^2 + y^2} \\ x = |z| \cos \theta, \quad y = |z| \sin \theta, \quad \theta = \tan^{-1} \frac{y}{x} \end{cases}$$

$$z = |z| (\cos \theta + j \sin \theta) = |z| e^{j\theta}$$

$$z_1 + z_2 = (x_1 \pm x_2) + j(y_1 \pm y_2)$$

$$z_1 \cdot z_2 = |z_1| |z_2| e^{j(\theta_1 + \theta_2)}$$


$$z_1 / z_2 = |z_1| / |z_2| e^{j(\theta_1 - \theta_2)}$$

A3 Euler's identity

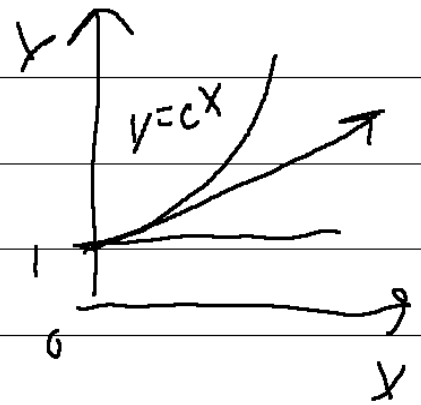(1) Taylor's Expansion

① Expression of a fct. by indefinite sums of many terms

(c.g.) $e^x \approx 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$



② $e^a \approx 1^{st} + 2^{nd} + 3^{rd} + \dots$

$e^{ja} \approx (1^{st} \cdot Re + 1^{st} \cdot Im) + (2^{nd} Re + 2^{nd} Im) + (3^{rd} Re + 3^{rd} Im) + \dots \approx \cos a + j \sin a$

(2) Euler's identity, ($\sin \leftrightarrow \exp$)

① $e^{j\omega t} = \cos \omega t + j \sin \omega t$ (i.e. $\cos \omega t = \text{Re}\{e^{j\omega t}\}$, $\sin \omega t = \text{Im}\{e^{j\omega t}\}$)
 $e^{-j\omega t} = \cos \omega t - j \sin \omega t$

② $\cos \omega t = (e^{j\omega t} + e^{-j\omega t})/2$
 $\sin \omega t = (e^{j\omega t} - e^{-j\omega t})/j2$

③ magnitude (length): $|e^{j\omega t}| = \sqrt{\sin^2 \omega t + \cos^2 \omega t} = 1$





7.5 Step Response (driven RC circuit)

(1) Complete Response

- ① Natural response (source free), $v_n(t)$
- ② Particular response (driven, forced) $v_p(t)$
- ③ Complete response:

$$\begin{aligned}
 v(t) &= v_p(t) + v_n(t) = v_p(t) + Ke^{st} \\
 &= v_p(t) + v_n(0^+)e^{st}, \text{ where } K = v_n(0^+) \\
 &= v_p(t) + [v(0^+) - v_p(0^+)]e^{st}, \text{ where} \\
 v(0^+) &= v_n(0^+) + v_p(0^+)
 \end{aligned}$$


(2) Constant Sources

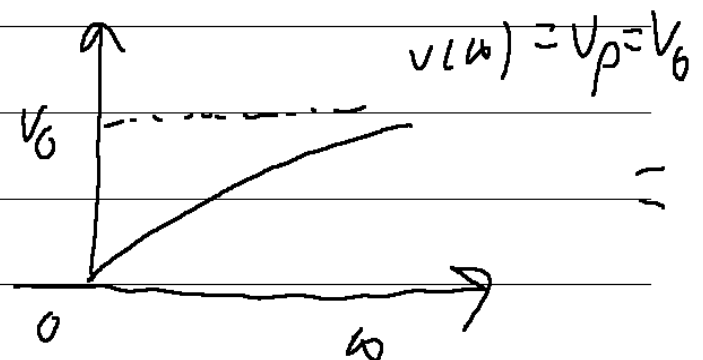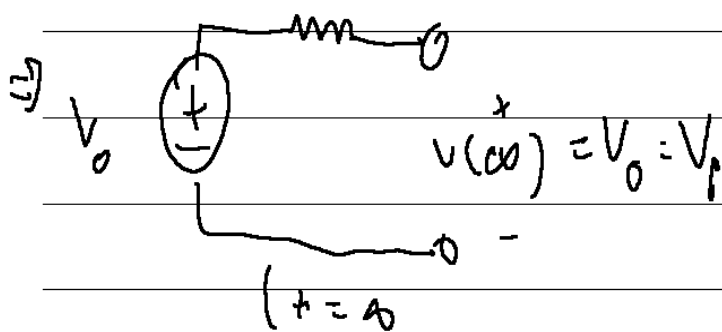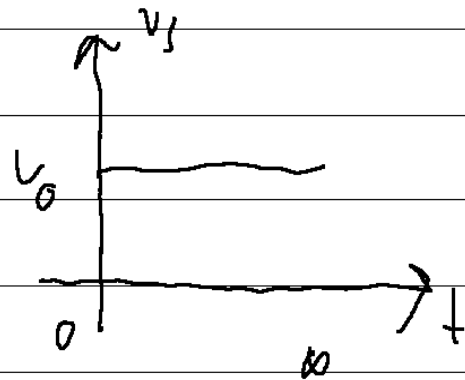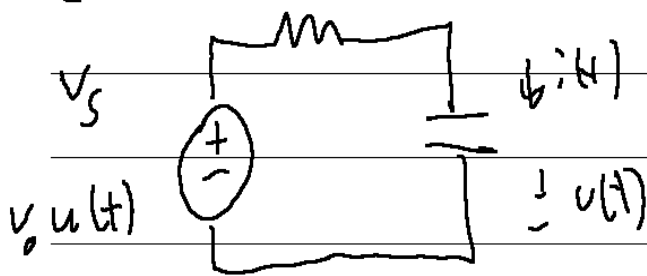

$$① v_p = v(\infty) = v_0$$

$$② v(t) = v(\infty) + [v(0^+) - v(\infty)]e^{st}$$

③ Capacitor behavior @ $t = \infty$

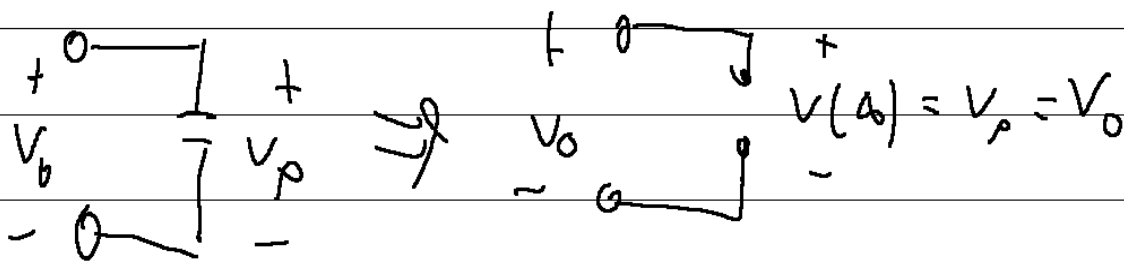

only V_p survived @ $t = \infty$, $i(\infty) = C \frac{dv_p}{dt} = 0$ (open-ckt)
(V_n died off soon)

(3) Diff. eq (constant, expon, sine sources)

① General form of natural response






$$V_n(t) = K e^{st}$$

② General form of natural response

$$V_p(t) = \begin{cases} A e^0 & \text{(for constant sources, } A e^{s_p t}, s_p = 0) \\ A e^{s_p t} & \text{(for expon. sources: } s_p \neq 0) \\ A t \cdot e^{s_p t} & \text{(for expon. source: } s_p = 0) \\ \text{Re} \{ A e^{i s_p t} \} & \text{(for sine sources)} \end{cases}$$

7.6



7.6 Step Response (Driven RL Circuit)

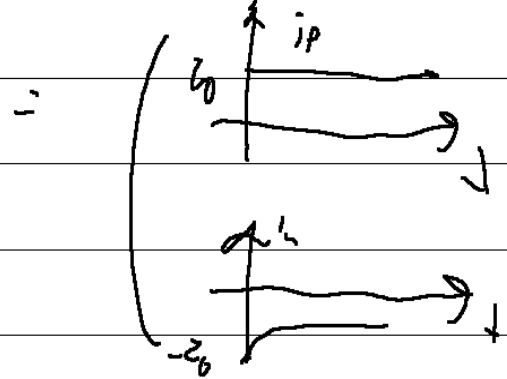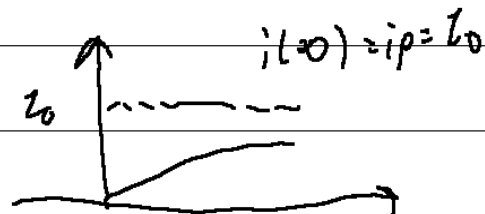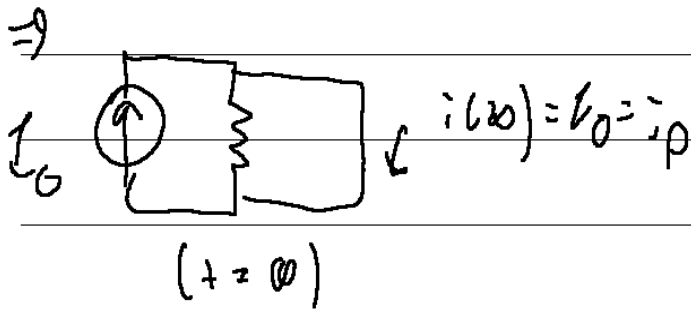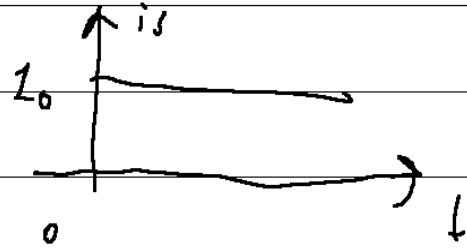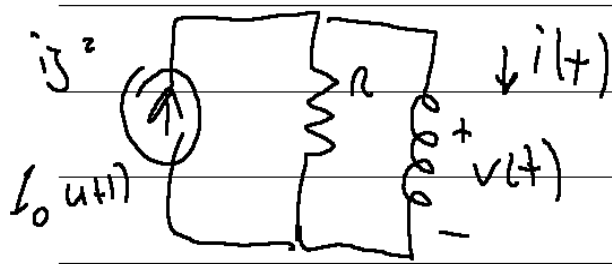

① $i_p = i(\infty)$


② $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$

③ Inductor behavior @ $t = 0$

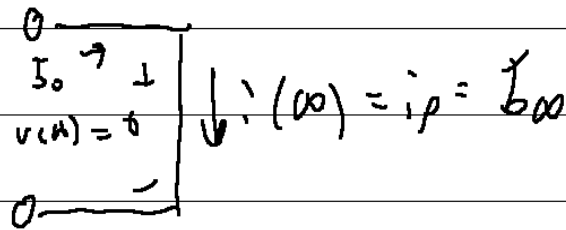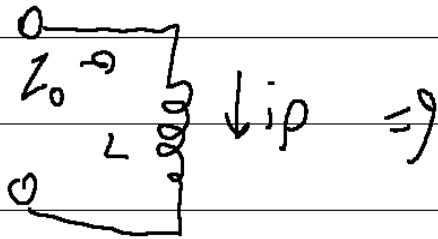

Ch. 8 Second Order Circuits

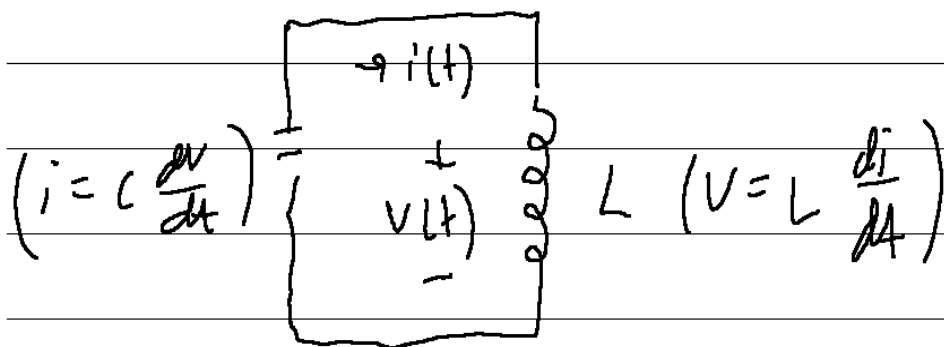(1) Two kinds of energy storage devices (L, C) in a network



(LC resonant tank)


(2) Diff. eq with two roots (s_1, s_2 : real, complex)

① Undamped: sinusoidal (oscillation)

② Underdamped: attenuating oscillation

③ Critically damped: intermediate

④ overdamped: asymptotic

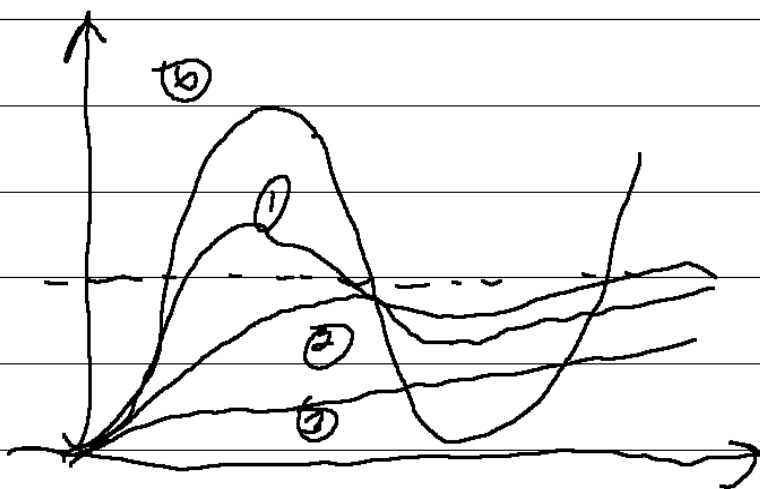

8.3 Source-Free Series RLC


(1) Diff eq

(KVL)

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_0^t i(\lambda) d\lambda = 0 \quad (t > 0)$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$
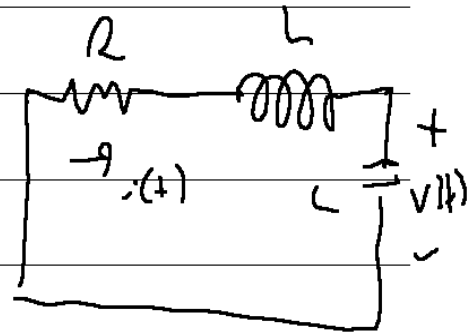
$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad \Rightarrow \quad s^2 + 2\alpha s + \omega_0^2 = 0$$



$$i(0^-) = i(0^+) = I_0$$

$$v(0^-) = v(0^+) = V_0$$

$$s_1, s_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\left(\begin{array}{l} = -\alpha \pm \sqrt{-\omega_0^2 - \alpha^2} \\ = -\alpha \pm j\omega_d \end{array} \right)$$

s_1, s_2 : natural freq.
 $\alpha = \frac{R}{2L}$: damping factor
 $\omega_0 = \sqrt{\frac{1}{LC}}$: resonant freq.
 (undamped natural freq.)
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$: damping freq.
 (damped natural freq.)

(2) General solution form

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{linear combination})$$

① overdamped ($\alpha > \omega_0$; $C > 4L/R^2$)

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (s_1, s_2: \text{real numbers})$$

② critically damped ($\alpha = \omega_0$; $C = 4L/R^2$)

$$i(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (s_1 = s_2 = -\alpha: \text{one real number})$$

③ underdamped ($\alpha < \omega_0$; $C < 4L/R^2$)


8.1 Source-free parallel RLL

(1) Diff eq.

$$(1 \text{ L } 1 \text{ L}) \quad L \frac{dv}{dt} + \frac{v}{2} + \frac{1}{L} \int_{-\infty}^t v(\lambda) d\lambda = 0 \quad (t \geq 0)$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RL} \frac{dv}{dt} + \frac{1}{LC} v = 0$$
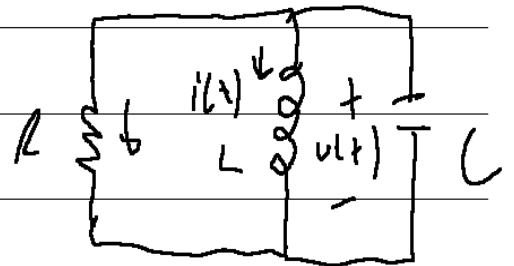
$$s^2 + \frac{1}{RL} s + \frac{1}{LC} \neq 0 \rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$



$$i(0^-) = i(0^+) = I_0$$

$$v(0^-) = v(0^+) = 0$$


(2) General Solution form

(same as those of source-free series RLL)

(3)

8.5 Step Responses of Series RLC

(1) Diff eq

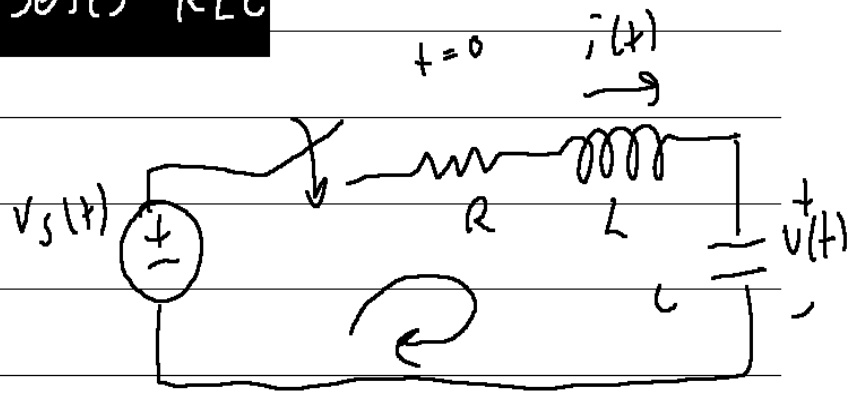

(KVL) $L \frac{di}{dt} + Ri + v = v_s(t)$

$\left(i = C \frac{dv}{dt} \right) \quad \left(v = \frac{1}{C} \int_{-\infty}^t i(\lambda) d\lambda \right)$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{v_s}{L} \quad (i)$$

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{v_s}{LC} \quad (v)$$

(2) Complete Responses

① Overdamp: $v(t) = v_p(t) + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2})$

② Critical damp: $v(t) = v_p(t) + (A_1 + A_2 t) e^{-\alpha t} \quad (s = -\alpha)$

③ Underdamp: $v(t) = v_p(t) + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (s = -\alpha \pm j\omega_d)$


(3) Particular responses

$$v_p(t) = A \text{ (const. input)}$$

$$= A e^{s_p t} \text{ (exp. input: } s \neq s_p)$$

$$= A t e^{s_p t} \text{ (exp. input: } s = s_p)$$

$$= R_c \{ e^{s_1 t} \}$$

 

Exam 4 Answer Key

1a)

$$V(0^-) = V(0^+) = 0 \text{ [V]}$$

$$b) \text{ KCL } \frac{1}{10} \frac{dv}{dt} - 4ib - ib = 0 \quad (ib = \frac{v_s - v}{10})$$

$$\frac{dv}{dt} + 10V = 10V_s = 10 \times 100e^{-5t}$$

$$c) \quad s + 10 = 0 \quad (s = -10)$$

$$\rightarrow V_h(t) = Ke^{-10t} \text{ [V]}$$

$$v_p = Ae^{-5t}, \quad v_p' = -5Ae^{-5t}$$

$$d) \text{ Diff eq } -5Ae^{-5t} + 10Ae^{-5t} = 1,000e^{-5t}$$

$$A = 200$$


$$\rightarrow \underline{V_p(t) = 200e^{-5t} \text{ [V]}}$$

$$e) \quad V(t) = V_h + V_p = Ke^{-10t} + 200e^{-5t}$$

$$V(0^+) = Ke^0 + 200e^0 = 0 \quad (K = -200)$$

$$\rightarrow V(t)$$

2) a)

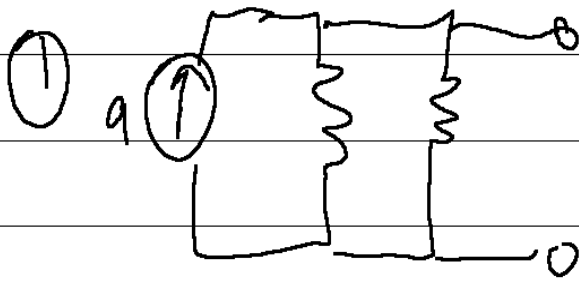


$$i_s = 24/24 = 1$$

$$R_p = 24/24 = 12$$

$$V_s = 9 \times 12 = 108$$

$$R_s = 12$$


b)

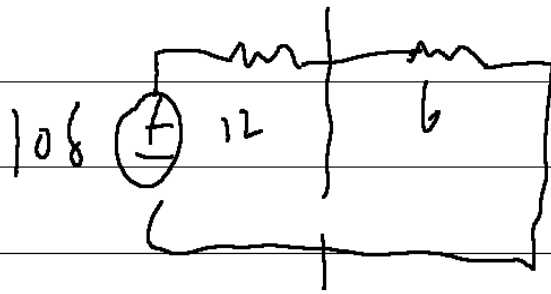

$$i(0^-) = \frac{108}{(12+6)} = 6 = i(0^+) [A]$$

c) (KVL) $3 \frac{di}{dt} + 12i = 108$

$$\frac{di}{dt} + 4i = 36$$

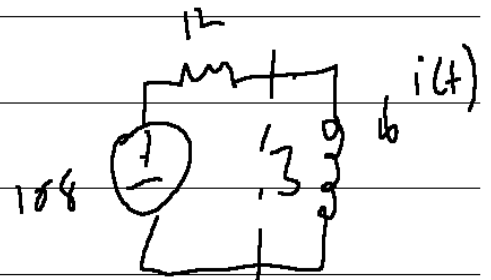


$$s + 4 = 0 \rightarrow s = -4 \quad \tau = -\frac{1}{s} = \frac{1}{4} \text{ (sec)}$$

d)

$$\text{OR } \tau = \frac{L_{eq}}{R_{eq}} = \frac{3}{12} = \frac{1}{4}$$

e)

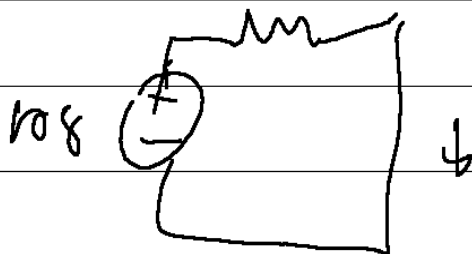

$$i(0) = \frac{108}{12} = 9 = i_n [A]$$

3a)

(1466)

$$2 \frac{dv}{dt} + dv + 8 \int_{-\infty}^t v(\tau) d\tau = 0$$

$$\frac{d^2 v}{dt^2} + 4 \frac{dv}{dt} + 4v = 0$$

$$b) \quad s^2 + 4s + 4 = 0 \quad (s = -2)$$

$$\rightarrow v_h(t) = (A_1 + A_2 t) e^{-2t} [v] \quad (-v(t))$$

c) critically damped

$$d) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{8} \times 2}} = 2 [42]$$

$$e) \quad v(0^+) = (A_1 + 0) e^0 = 2 \quad \Rightarrow A_1 = 2$$

$$v'(t) = A_2 e^{-2t} - 2(A_1 + A_2 t) e^{-2t}$$


$$v'(0^+) = A_2 e^0 - 2(A_1 + 0) e^0 = A_2 - 2A_1 = A_2 - 4$$

$$\text{Dip} \text{ c} \text{ a } t=0^+, \quad v'(0^+) + 6(v(0^+))' i(t) = 0$$

$$2(A_2 - 4) + 8 \times 2 \times 2 = 0$$

$$\Rightarrow \underline{A_2 = -6}$$

u a)

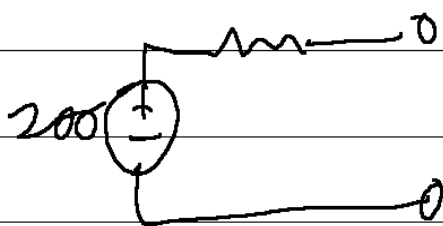

$$b) \quad (1 \text{ kV}) \quad s \frac{d^2}{dt^2} + 60i + 250 \int_{-\infty}^t i(\lambda) dV = V_s$$

$$\frac{d^2 i}{dt^2} + 10 \frac{di}{dt} + 60i = \frac{1}{5} \frac{dV_s}{dt} = 0$$

$$s^2 + 10s + 60 = 0 \quad (s = -5 \pm j5)$$

$$c) \quad i_{in}(t) = (A_1 \cos st + A_2 \sin st) e^{-5t} \quad [A]$$

$$d) \quad i_r = A \quad i_y = 0 \quad i_p = 0$$

2nd order diff eq

$$0 + 10 \times 0 + 60A = 0$$

$$A = 0 = i_r(t) \quad [A]$$

Final Exam prep

• 8 of 10 problems